

National Exam May, 2016

07-Elec-A1 Circuits

3 hours duration

NOTES:

1. **No questions to be asked.** If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any logical assumptions made.
2. Candidates may use one of two calculators, a Casio or Sharp . **No programmable models** are allowed.
3. This is a **closed book** examination.
4. Any **five questions** constitute a complete paper. Please **indicate in the front page of your answer book which questions you want to be marked.** If not indicated, only the first five questions as they appear in your answer book will be marked.
5. All questions are of equal value. **Part marks will be given for right procedures.**
6. **Some useful equations and transforms** are given in the last page of this question paper.

- Q1:** (a) In the circuit shown in Figure-1, if the equivalent resistance at terminals A-B, $R_{AB} = 5\Omega$, calculate value of the unknown resistance, R. [10]
 (b) If a 10V dc source is connected to terminals A-B, calculate the current I_R and also calculate the power supplied by the 10V source to the whole circuit. [5+5]

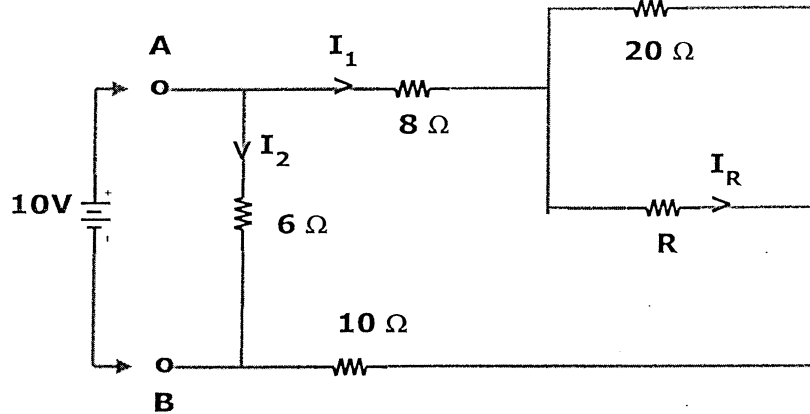


Figure-1

- Q2:** For the circuit with a controlled voltage source shown in Figure-2, (a) calculate the Thevenin's equivalent circuit (V_{th} and R_{th}) at terminals a-b. (b) What should be the Load resistance, R_L which must be connected for maximum power dissipation? (c) calculate this maximum power dissipation in R_L . [10+4+6]

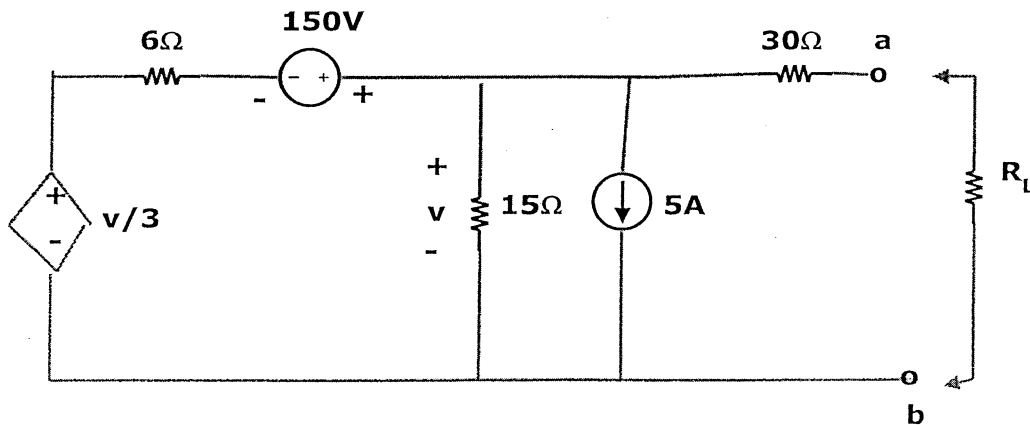


Figure-2

Q3: For the Circuit shown in Figure-3, the switch was in position-a for a long time, at $t = 0$, it is moved to position-b . Calculate (i) $V_c(0^+)$ at $t = 0^+$, (ii) $V_c(t)$ at $t \geq 0$, and(iii) calculate $V_c(2)$ at $t = 2$ sec. [5+10+5]

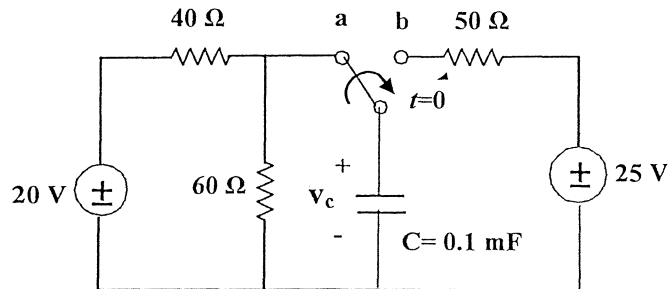


Figure-3

Q4: In the circuit shown in Figure-4 below, $R_1= 2\Omega$, $R_2= 5 \Omega$, $L= 2H$, $C=0.1F$, $v_s(t) = 20 \cos (5t +30^0)V$, and $i_s(t)= 15 \sin(5t+20^0) A$.

- (a) Write the mesh current equations in phasor for the directions of the mesh currents shown. [10]
- (b) Solve the mesh currents I_1 and I_2 . [5]
- (c) Calculate the voltage $V_0(t)$, as shown in the diagram. [5]

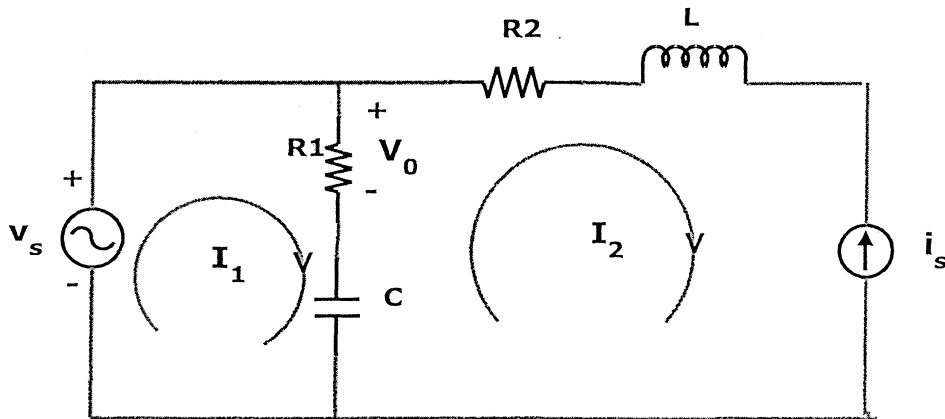


Figure-4

Q5: In the circuit shown in Figure-5 below, the supply voltage is shown in RMS as $110\angle 0^\circ$ V.

- (a) Calculate the supply current, I_s . [4]
 (b) Draw the phasor diagram of V_s and I_s . [4]
 (c) Calculate the power factor of operation of the source, V_s . [4]
 (d) What the complex power S , Real Power P , and Reactive Power, Q of the source? [2+3+3]

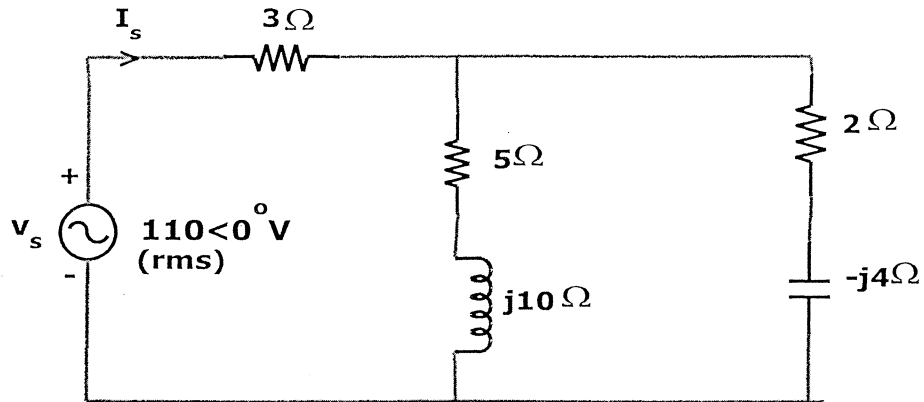


Figure-5

Q6: For the circuit shown in Figure-6, the switch was open and initial voltage on the capacitor, $V_C(0) = 4$ V, and the initial current in the inductor, $i_L(0) = 1$ A. At $t = 0$, the switch is closed.

- (a) Draw the Laplace equivalent circuit of the network at $t \geq 0$. [10]
 (b) If $V_s = 12$ V, $R = 5\ \Omega$, $L = 2$ H, and $C = 1$ F, calculate the voltage across the capacitor, $V_C(t)$ at $t \geq 0$. [10]

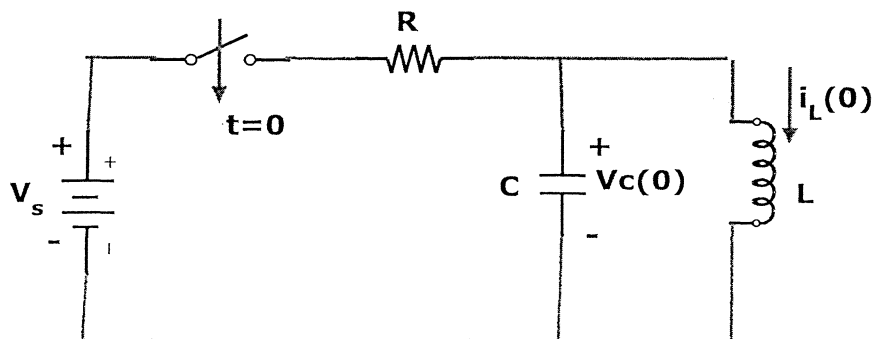
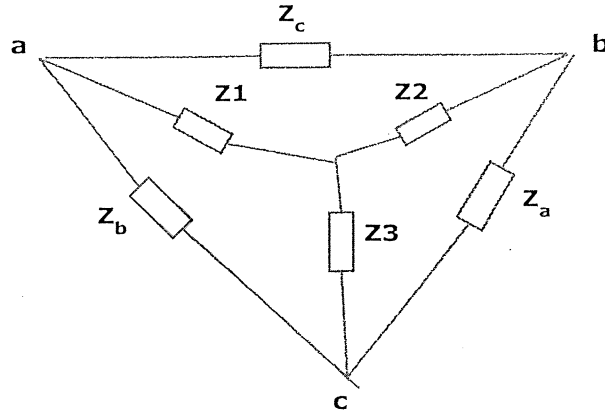


Figure-6

Appendix

Some useful Laplace Transforms:

<u>f(t)</u>	→	<u>F(s)</u>
$Ku(t)$		K/s
$\delta(t)$		1
t		$1/s^2$
$e^{-at} u(t)$		$1/(s+a)$
$\sin \omega t \cdot u(t)$		$\omega / (s^2 + \omega^2)$
$\cos \omega t \cdot u(t)$		$s / (s^2 + \omega^2)$
$e^{-\alpha t} \sin \omega t$		$\frac{\omega}{(s+\alpha)^2 + \omega^2}$
$e^{-\alpha t} \cos \omega t$		$\frac{(s+\alpha)}{(s+\alpha)^2 + \omega^2}$
$\frac{df(t)}{dt}$		$sF(s) - f(0^-)$
$\frac{d^2 f(t)}{dt^2}$		$s^2 F(s) - s f(0^-) - f'(0^-)$
$\int_{-\infty}^t f(q) dq$		$\frac{F(s)}{s} + \int_{-\infty}^0 f(q) dq$

Star – Delta conversion:

$$Z_1 = \frac{Z_b \cdot Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a \cdot Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a \cdot Z_b}{Z_a + Z_b + Z_c}$$

$$Z_a = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_3}$$

$$Z_b = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_1}$$