

National Exams December 2015

98-Comp-A1, Electronics

3 hours duration

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate is urged to indicate, with the answer, a clear statement of any assumptions made.
2. This is a OPEN BOOK exam.
Any non-communicating calculator is permitted.
3. FIVE (5) questions constitute a complete exam paper.
The first 5 questions as they appear in the answer book will be marked.
4. Each question is of equal value.

Question 1 (20 marks)

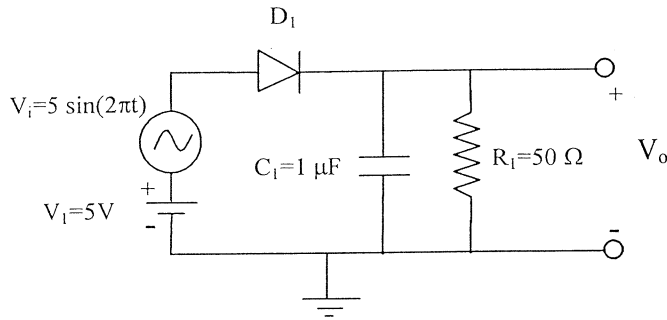


Figure 1. The diode has a voltage drop $V_D=0.7V$ in forward bias.

For the circuit shown in Figure 1:

- Sketch V_i and V_o as a function of time, indicating peak voltages.
- Find the maximum and minimum output voltage V_o .
- What is the peak current through R_1 ?

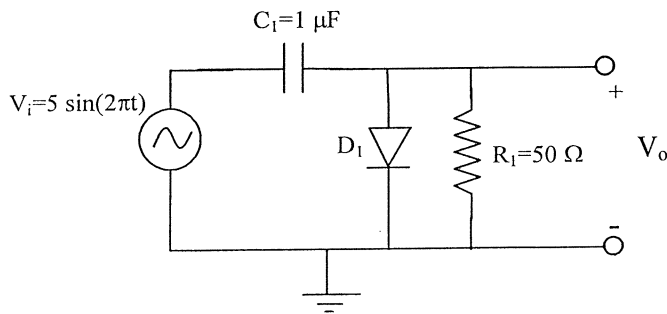


Figure 2. The diode has a voltage drop $V_D=0.7V$ in forward bias.

For the circuit shown in Figure 2:

- Sketch the output waveform $V_o(t)$ in steady state. Label peak voltages.

Question 2 (20 marks)

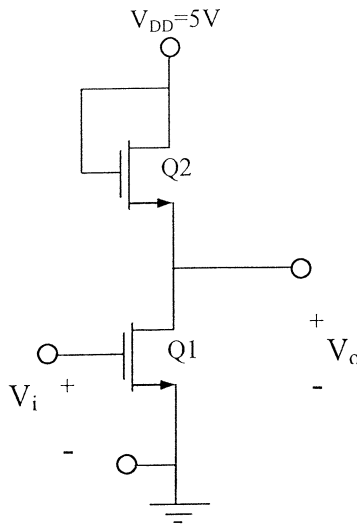


Figure 3. $k_n' = \mu_n C_{ox} = 1 \text{ mA/V}^2$, $W/L = 10$, $V_{tn} = 1\text{V}$, $|V_A| = 100\text{V}$

For the circuit shown in Figure 3:

- a) For $V_i = 2\text{V}$ what is the current through Q1?
- b) For $V_i = 2\text{V}$, what is V_o ?
- c) Draw a small signal equivalent model for the circuit.
- d) What is the small signal AC gain of the circuit?

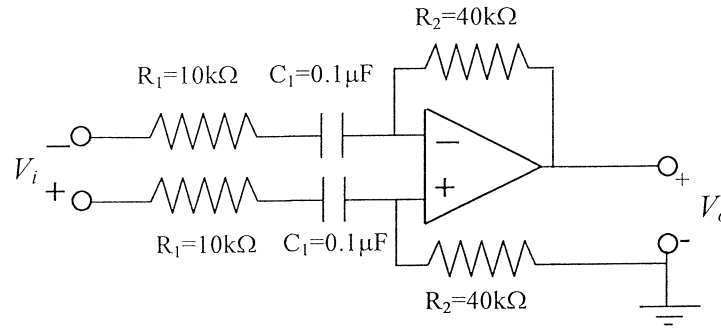
Question 3 (20 marks)

Figure 4.

For the circuit shown in Figure 4:

- Derive the transfer function $\frac{V_o(j\omega)}{V_i(j\omega)}$ for the circuit shown in Figure 4, assuming the op-amp is ideal.
- Sketch the frequency response, indicating 3dB frequencies for this circuit.
- If $V_i(t) = 10\sin(120\pi t)$ V, find $V_o(j\omega)$.
- If $V_i(t) = 10\sin(120\pi t)$ V, find $V_o(t)$.

Question 4(20 marks)

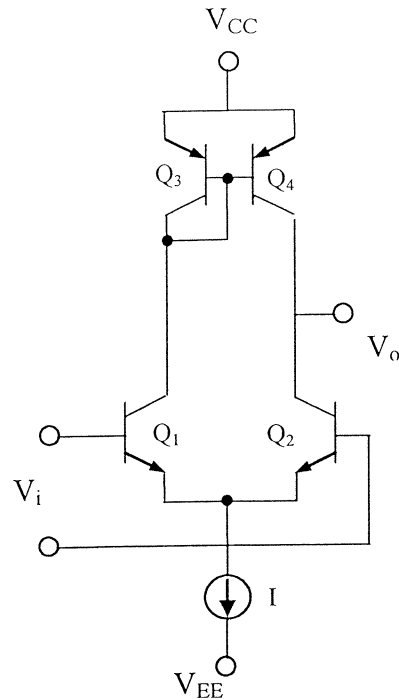


Figure 5. $I=0.2\text{mA}$, $\beta=100$, $V_A=100\text{V}$.

For the circuit shown in Figure 5:

- Find the input resistance R_i .
- Find the output resistance R_o .
- Find the amplifier transconductance G_m .
- Find the open-circuit voltage gain for the amplifier.

Question 5 (20 marks)

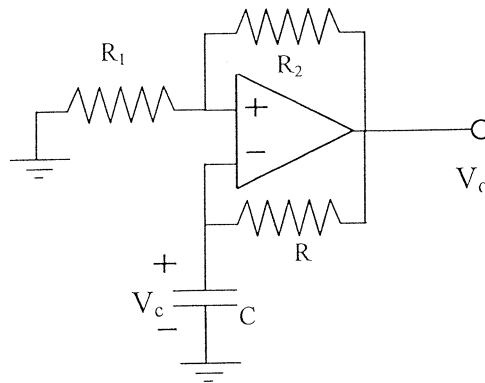


Figure 6. The op-amp saturation voltages are $\pm 12\text{V}$, $R_1=10\text{k}\Omega$, $R_2=R=100\text{k}\Omega$, $C=0.1\mu\text{F}$.

For the circuit shown in Figure 6:

- Explain the operation of this circuit.
- Sketch the waveforms $V_c(t)$ and $V_o(t)$.
- Find an expression for $V_c(t)$.
- Find the frequency of the output signal V_o .

Question 6 (20 marks)

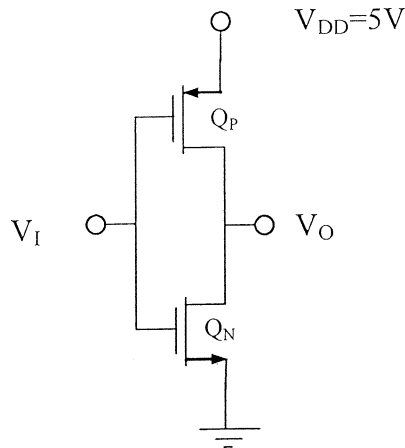


Figure 7. $k_n' = 50 \mu\text{A}/\text{V}^2$, $k_p' = 20 \mu\text{A}/\text{V}^2$, $V_{tn} = -V_{tp} = 1\text{V}$, $C_{ox} = 1\text{fF}/\mu\text{m}^2$, $V_{DD} = 5\text{V}$
 Gate-drain overlap $C_{gd} = 0.5\text{fF}/\mu\text{m}$, drain-body $C_{db} = 10\text{fF}$, wiring $C_{ox} = 5\text{fF}$.

- If the minimum gate length for this technology is $1 \mu\text{m}$, size Q_N and Q_P to obtain a symmetric transfer characteristic.
- Evaluate the propagation delay for this inverter driving a second identical inverter.

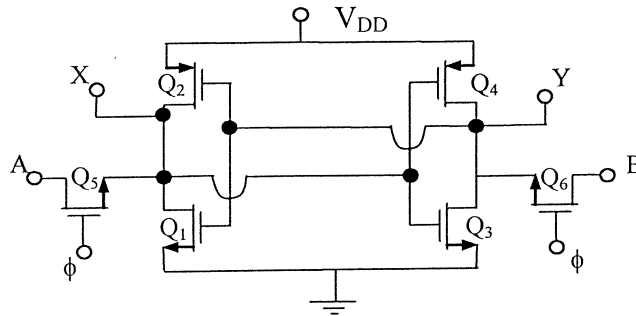


Figure 8.

For the circuit shown in Figure 8:

- Determine outputs X and Y for all possible inputs A and B . ϕ is a clock signal.
- If Q_1 and Q_2 are sized as in part a), find a minimum size for Q_5 and Q_6 that will ensure X can be pulled down to $V_{DD}/2$ or lower.

Question 7 (20 marks)

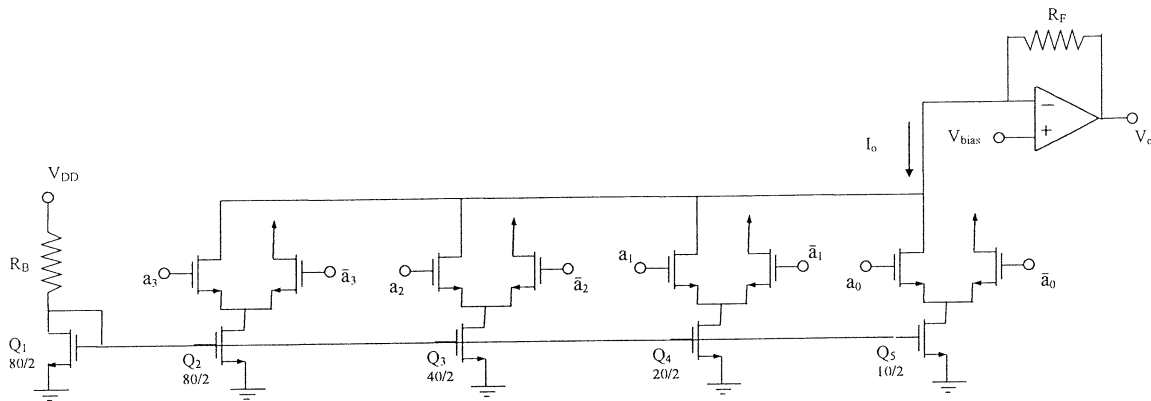


Figure 9. $R_B=20k\Omega$, $R_F=5k\Omega$, $V_{DD}=5V$, $V_{bias}=1V$
 $V_t=0.8V$, $k'=40 \mu A/V^2$. Transistor dimensions in μm .

- What is a common name for the circuit shown in Figure 9? Briefly explain how it works.
- Calculate the drain current for Q_1 (choose a starting value for the gate voltage and iterate to a solution).
- If a_3 - a_0 are connected to V_{DD} , find I_0 . For each value of $A_{in}=0000$ to $A_{in}=1111$ determine the output V_o .
- What are the limitations of the application of this circuit?

Marking Scheme

1. 20 marks total (4 parts, 5 marks each)
2. 20 marks total (4 parts, 5 marks each)
3. 20 marks total (4 parts, 5 marks each)
4. 20 marks total (4 parts, 5 marks each)
5. 20 marks total (4 parts, 5 marks each)
6. 20 marks total (4 parts, 5 marks each)
7. 20 marks total (4 parts, 5 marks each)