

# National Exams May 2019

16-Elec-B5, Advanced Electronics

3 hours duration

## Notes:

1. If any doubt exists as to the interpretation of any question, the candidate is urged to submit, within their answer, a clear statement of any assumptions made.
2. This is a **CLOSED BOOK EXAM**. One of two calculators is permitted - any Casio or Sharp approved model.
3. Answer all **FIVE** (5) questions.
4. All questions are worth 20 marks each.
5. Please start each question on a new page and clearly identify the question number and part number, e.g. Q4(a).
6. In schematics, ground and chassis may be assumed to be common, unless specifically stated otherwise.
7. Unless otherwise specified, assume that Op-Amps are ideal and that supply voltages are  $\pm 15V$ .
8. If questions require an answer in essay format, clarity and organization of the answer are important. Provide block diagrams and circuit schematics whenever necessary.


**QUESTION (1)**

An analog signal in the range 0 to +10 V is to be converted to an 8-bit digital signal.

- a) What is the resolution of the conversion in volts? (4 points)
- b) What is the digital representation of an input of 6 V? (4 points)
- c) What is the representation of an input of 6.2 V? (4 points)
- d) What is the error made in the quantization of 6.2 V in absolute terms and in percentage of the input? And as a percent of full scale? (4 points)
- e) What is the largest possible quantization error as a percentage of full scale? (4 points)

 **QUESTION (2)**

The following circuit is a class AB power amplifier. The output stage is essentially comprised of two common source amplifiers. The two error amplifiers are used to provide negative feedback to lower the output resistance of this output stage.




Given the followings:

- i) Transistors  $M_1$  and  $M_2$  are matched such that  $K_n = K_p$ , and  $V_{Tn} = |V_{Tp}|$
- ii)  $I_Q$  is the quiescent current for transistors  $M_1$  and  $M_2$  with zero input.
- iii)  $\mu$  is the finite gain of the error amplifiers.
- iv)  $R_L$  is the load resistance

- a) Derive an expression for the voltage gain  $v_{OUT}/v_{IN}$  of this amplifier? (12 points)
- b) What would be the expected gain? (2 points)
- c) What would be the gain error? (6 points)

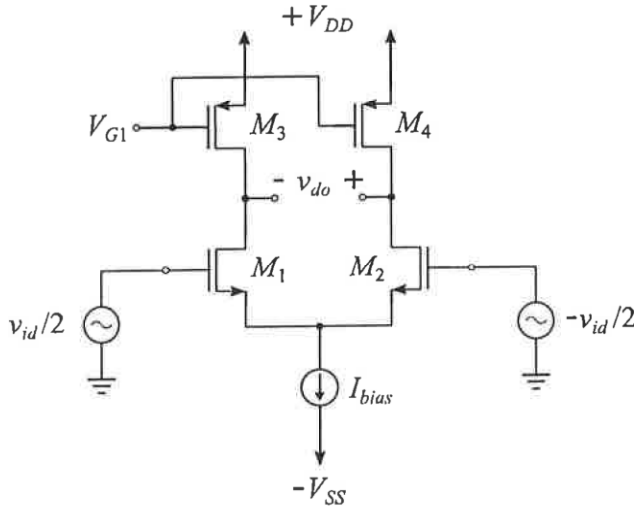**QUESTION (3)**

The following single stage differential amplifier circuit is designed for a 0.18 μm CMOS technology.



Given:  $V_{DD} = |V_{SS}| = 1.5 \text{ V}$ ,  $|V_{TH}| = 0.5 \text{ V}$ ,  
 $L = 0.36 \text{ } \mu\text{m}$  (for all transistors),  
 $\mu_n C_{ox} = 4\mu_p C_{ox} = 400 \text{ } \mu\text{A/V}^2$ ,  
 and  $\lambda = 0.2$

- a) For a bias current of  $I_{bias} = 200 \text{ } \mu\text{A}$  and over drive voltage  $|V_{ov}| = 0.2 \text{ V}$  for all transistors, determine the  $W/L$  ratios for  $M_1$ ,  $M_2$ ,  $M_3$ , and  $M_4$ . (10 points)
- b) Determine the small signal differential gain  $v_{do}/v_{id}$  for this design. (10 points)

Useful formulae: for n-channel MOSFET

$$i_{DS} = K \left[ (v_{GS} - V_{TH})v_{DS} - \frac{1}{2}v_{DS}^2 \right] \quad \text{triode region}$$

$$i_{DS} = \frac{1}{2}K (v_{GS} - V_{TH})^2 (1 + \lambda v_{DS}) \quad \text{saturation region}$$

$$V_{ov} = V_{GS} - V_{TH} \quad \text{overdrive voltage}$$


where

$$K = K' \left( \frac{W}{L} \right) = \mu C_{ox} \left( \frac{W}{L} \right)$$

$$V_A = \frac{1}{\lambda}, \text{ and } V_A = V_A' L, \quad r_o = \frac{1}{\lambda I_D}$$

 **QUESTION (4)**

This following current mirror circuit is used to provide bias currents  $I_3$  and  $I_4$  to other circuit blocks.




Given:  $V_{DD} = 3.0 \text{ V}$ ,  $|V_{TH}| = 0.5 \text{ V}$ ,  
 $L = 0.36 \text{ } \mu\text{m}$  (for the  $p$ -channel transistors),  
 $\mu_n C_{ox} = 4\mu_p C_{ox} = 400 \text{ } \mu\text{A/V}^2$ ,  
 and  $\lambda = 0.2$

- a) For a bias current of  $I_{bias} = 200 \text{ } \mu\text{A}$  and over drive voltage  $|V_{ov}| = 0.3 \text{ V}$  for all the  $p$ -channel transistors, determine the  $W/L$  ratios for  $M_1$ , and  $M_2$ . Note that the channel length for transistor  $M_1$  can be  $0.36 \text{ } \mu\text{m}$  or longer. (8 points)
- b) Determine the  $W/L$  ratios for  $M_3$ , and  $M_4$  for  $I_3 = 4 \times I_4 = 8 \times I_{bias}$ . (2 points)
- c) Determine the variation in  $I_3$  if the voltage  $V_3$  swings from 0 to 1.5 V. (10 points)

 **QUESTION (5)**

The following common emitter amplifier is already biased properly. Determine the appropriate values for  $C_{C1}$ ,  $C_{C2}$ ,  $C_E$  to provide a lower cutoff frequency of  $f_L = 100$  Hz. Which capacitor dominates this corner frequency? (20 points)



Given:  $R_{B1} = 180 \text{ k}\Omega$ ,  
 $R_{B2} = 270 \text{ k}\Omega$ ,  
 $R_S = 5 \text{ k}\Omega$ ,  
 $R_C = 8 \text{ k}\Omega$ ,  
 $R_E = 2 \text{ k}\Omega$ ,  
 $R_L = 5 \text{ k}\Omega$ ,  
 $\beta = 100$ ,  
 $g_m = 40 \text{ mA/V}$ , and  
 $r_\pi = 2.5 \text{ k}\Omega$ .