

National Exam December, 2013

07-Elec-A1 Circuits

3 hours duration

NOTES:

1. **No questions to be asked.** If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any logical assumptions made.
2. Candidates may use one of two calculators, a Casio FX or Sharp EL . **No programmable models** are allowed.
3. This is a **closed book** examination.
4. Any **five questions** constitute a complete paper. Please indicate in the front page of your answer book which questions you want to be marked. **If not indicated, only the first five questions as they appear in your answer book will be marked.**
5. All questions are of equal value.
6. **Laplace Table** is given in the last page of this question paper.

Q1: (a) Write the node voltage equations at nodes 1 and 2 of the dc circuit shown in Figure-1.

Solve node voltages V_1 and V_2 . [12]

(b) After solving the node voltages, calculate the power dissipations in 5Ω and 4Ω resistances. [8]

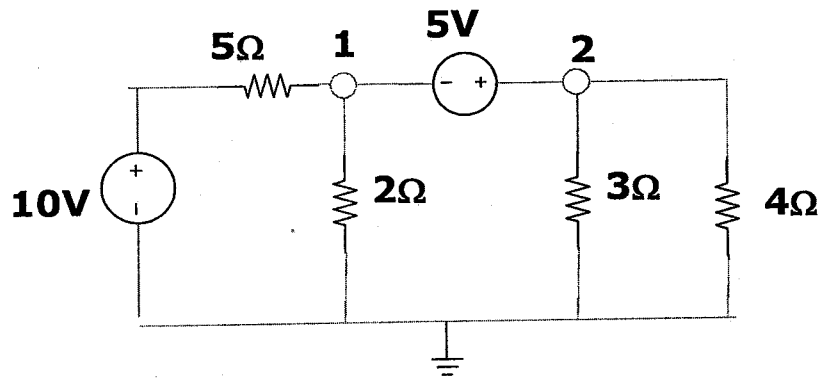


Figure-1

Q2: In the circuit shown in Figure-2, the switch was in position-a for a long time. At time $t=0$, the switch is moved to position-b.

(i) At $t=0^+$, calculate $V_c (+)$. [5]

(ii) Solve $V_c (t)$ at $t \geq 0$. [10]

(iii) Find V_c at $t = 2$ sec. [5]

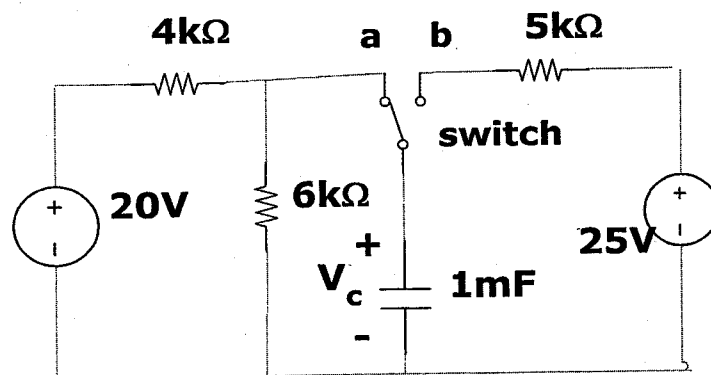


Figure-2

- Q3: (a) Write the current mesh equations of the circuit shown in Figure-3. [10]
 (b) Solve the mesh currents. [5]
 (c) After solving the mesh currents, calculate the voltage, V_o across the resistance 4Ω . [5]

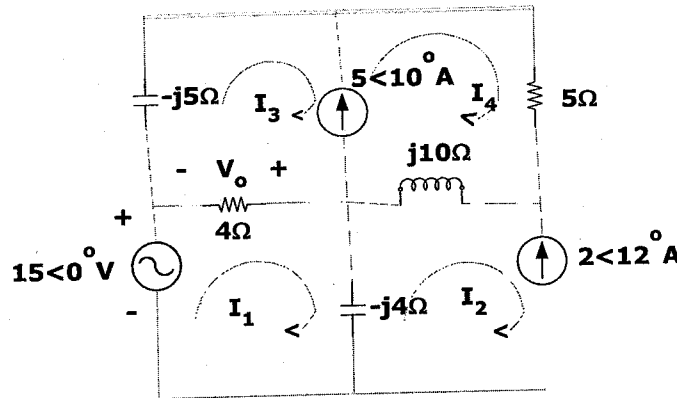


Figure-3

- Q4: (a) Calculate the Thevenin's equivalent circuit (V_{th} and Z_{th}) at terminals A-B of the circuit shown in Figure-4. [12]
 (b) What should be the value of load impedance, Z_{load} at A-B to get maximum Power output in Z_{load} . [2]
 (c) What is the maximum power dissipation in the load Z_{load} ? [6]

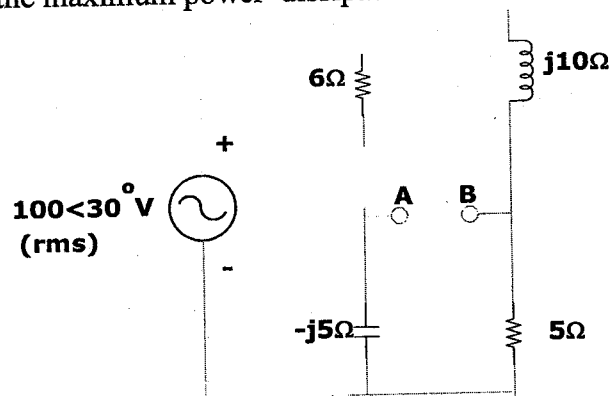


Figure-4

- Q5: (a) Calculate the resonance frequency, f_0 of the circuit shown in Figure-5. [12]
 (b) Calculate the cut-off frequencies f_1 and f_2 of the circuit. [8]

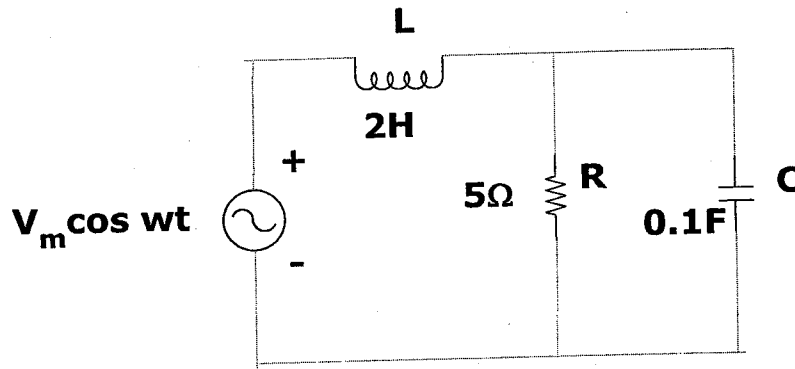


Figure-5

- Q6: The circuit shown in Figure-6 has initial capacitor voltage of $8V$, and initial Inductor current of $4A$.

- (a) Draw Laplace transformed circuit of the network. [10]
 (b) Calculate Laplace inductor current, $I_L(s)$. [5]
 (c) Solve $i_L(t)$. [5]

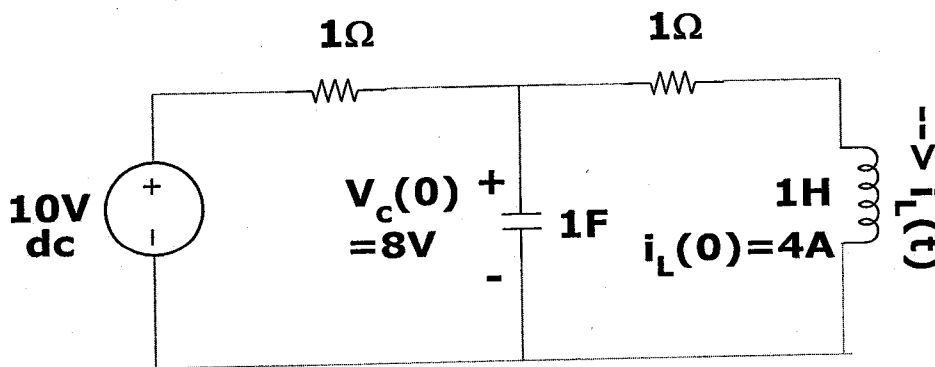


Figure-6

Appendix

Some useful Laplace Transforms:

<u>f(t)</u>	→	<u>F(s)</u>
$Ku(t)$		K/s
t^n		$\frac{n!}{s^{n+1}}$
$e^{-at} u(t)$		$1/(s+a)$
$\sin \omega t \cdot u(t)$		$\omega / (s^2 + \omega^2)$
$\cos \omega t \cdot u(t)$		$s / (s^2 + \omega^2)$
$e^{-at} \sin \omega t$		$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos \omega t$		$\frac{(s+a)}{(s+a)^2 + \omega^2}$
$\frac{df(t)}{dt}$		$sF(s) - f(0^-)$
$\frac{d^2 f(t)}{dt^2}$		$s^2 F(s) - s f(0^-) - f'(0^-)$
$\int_{-\infty}^t f(q) dq$		$\frac{F(s)}{s} + \int_{-\infty}^0 f(q) dq$