

National Exams December 2016

98-Comp-A1, Electronics

3 hours duration

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate is urged to indicate, with the answer, a clear statement of any assumptions made.
2. This is a OPEN BOOK exam.
Any non-communicating calculator is permitted.
3. FIVE (5) questions constitute a complete exam paper.
The first 5 questions as they appear in the answer book will be marked.
4. Each question is of equal value.

 
Question 1 (20 marks)

Figure 1. All diodes have a forward voltage drop $V_D=0.7\text{V}$. Diode D_2 has a maximum reverse voltage of 4.3V .

The circuit shown in Figure 1 is in steady state:

- Sketch V_1 and V_o as a function of time, indicating peak voltages.
- Sketch V_R , as a function of time, indicating peak voltages.
- What is the peak current through R_1 ?
- Which diode has the largest peak power dissipation? What power rating would you choose for this diode?

Question 2 (20 marks)

 


Figure 2. $I_{ref}=100 \mu A$, $k_n'=\mu_n C_{ox}=100 \mu A/V^2$, $k_p'=50 \mu A/V^2$, $W/L=50$, $|V_t|=1V$, $V_A=50V$ and $\chi=0.2$. ($W/L=5$ for all transistors).

For the circuit shown in Figure 2:

- Draw a small signal equivalent model for the circuit.
- Find the input resistance of the circuit.
- What is the small signal AC voltage gain of the circuit?

Question 3 (20 marks)

 


Figure 3.

For the circuit shown in Figure 3:

- Find the circuit DC gain.
- Find the circuit AC gain.
- Sketch the frequency response, indicating 3dB frequencies for this circuit.
- If the op-amp output is limited by the supply to $\pm 15\text{V}$, and $V_i(t) = A \sin(120\pi t)$ V, find a maximum value of A such that $V_o(t)$ is not clipped or distorted..

Question 4(20 marks)

 


Figure 4. $I=0.2\text{mA}$, $\beta=100$, $V_A=100\text{V}$.

For the circuit shown in Figure 4:

- Draw the small signal equivalent circuit.
- Find the small signal input resistance R_i and output resistance R_o .
- Find the open circuit voltage gain for the amplifier and the loaded voltage gain.

Question 5 (20 marks)

 


Figure 5. $R=10\text{k}\Omega$, $C=0.1\mu\text{F}$

For the circuit shown in Figure 5:

- What is the condition for oscillation of the output?
- What are the frequency and amplitude of the output signal?
- Choose component values R_1 and R_2 to sustain oscillation.

Question 6 (20 marks)

Consider a CMOS inverter with parameters $k_n' = \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $k_p' = 50 \mu\text{A}/\text{V}^2$, $|V_t| = 1\text{V}$, $V_{DD} = 5\text{V}$.

- a) Synthesize a CMOS logic circuit that will realize the Boolean function
$$F = \overline{D + A \cdot (B + C)}.$$
- b) An inverter in this technology with a minimum gate length $L = 0.5 \mu\text{m}$ has a symmetric transfer function for NMOS $W/L = 2$ and PMOS $W/L = 5$. Choose sizes for the transistors in the gate design from a) in order to maintain a symmetric characteristic.
- c) If the gate must drive a capacitance of 1pF , estimate the propagation delay for this circuit?

Question 7 (20 marks)

 


Figure 6.

- Write expressions relating V_1 , V_2 , and V_3 to V_{in} .
- Write expressions relating V_4 and V_5 to V_1 , V_2 , and V_3 .
- If 4 output bits are needed, how many comparators would be required?
- What is the resolution (in volts) of this circuit?

Marking Scheme

1. 20 marks total (4 parts, 5 marks each)
2. 20 marks total (a. 7 marks, b. 5 marks, c. 8 marks)
3. 20 marks total (4 parts, 5 marks each)
4. 20 marks total (a. 7 marks, b. 6 marks, c. 7 marks)
5. 20 marks total (a. 10 marks, b. 5 marks, c. 5 marks)
6. 20 marks total (a. 7 marks, b. 6 marks, c. 7 marks)
7. 20 marks total (4 parts, 5 marks each)