

National Exams May 2018

16-Elec-A5, Electronics


3 hours duration

Notes:

1. If any doubt exists as to the interpretation of any question, the candidate is urged to submit, within their answer, a clear statement of any assumptions made.
2. This is a **CLOSED BOOK EXAM**.
One of two calculators is permitted - any Casio or Sharp approved model.
3. Answer all **FIVE** (5) questions.
4. All questions are worth 20 marks each.
5. Please start each question on a new page and clearly identify the question number and part number, e.g. Q4(a).
6. In schematics, ground and chassis may be assumed to be common, unless specifically stated otherwise.
7. Unless otherwise specified, assume that Op-Amps are ideal and that supply voltages are $\pm 15V$.
8. If questions require an answer in essay format, clarity and organization of the answer are important. Provide block diagrams and circuit schematics whenever necessary.

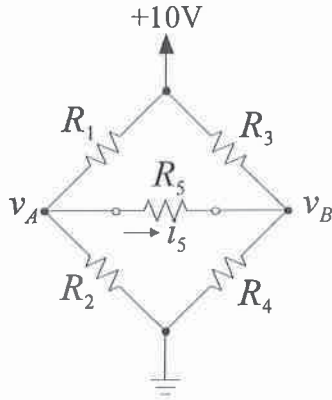
QUESTION (1)

In the following circuit, determine the current, i_5 flowing through and the voltage, v_{AB} across resistor R_5 . (20 points)




- Given:
- $R_1 = 1 \text{ k}\Omega$
 - $R_2 = 1.2 \text{ k}\Omega$
 - $R_3 = 9.1 \text{ k}\Omega$
 - $R_4 = 11 \text{ k}\Omega$
 - $R_5 = 2 \text{ k}\Omega$

QUESTION (2)

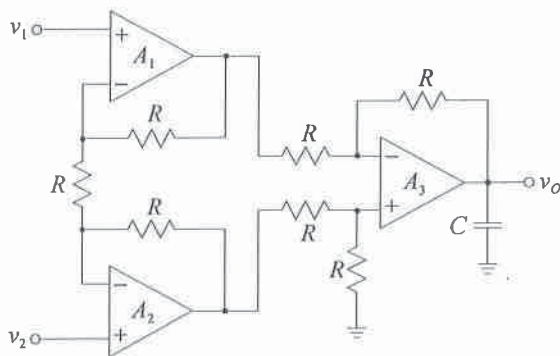


Given that all the op amps are ideal. The power supplies for op amps are $\pm 15\text{V}$. Also, $R = 10\text{k}\Omega$ and $C = 10\mu\text{F}$.

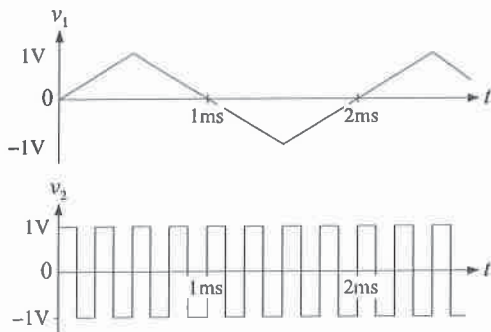- (a) Derive an expression for the output voltage v_o as a function of v_1 and v_2 . (10 points)
- (b) Sketch the output waveform accurately in your answer book. (10 points)



QUESTION (3)

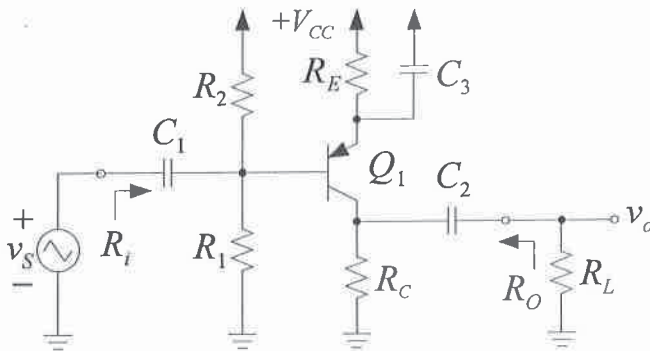

Assume that the BJT has the following characteristics:

- $\beta = 100$
- $V_{EB(on)} = 0.7V$
- $V_{EC(sat)} = 0.3V$
- $V_A = \infty$

Given: $V_{CC} = 10V$, $R_L = 10k\Omega$, and $R_E = 1k\Omega$,

a) Design this common emitter amplifier circuit to have the following specification:

- DC bias current, $I_E = 2mA$,
- A mid-band voltage gain $v_{out}/v_s = 100 V/V$
- Provide values for R_1 , R_2 , and R_C .

(15 points)

b) What is the equivalent output resistance, R_O ?


(2 points)

c) What is the maximum undistorted peak to peak output voltage swing at the output? (3 points)

QUESTION (4)

Solve for the currents I_1 , I_2 , and I_3 in the following diode circuit.

(20 points)

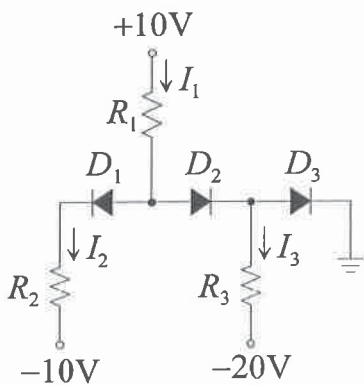

Given:

All diodes are ideal with 0.6V forward drop


$R_1 = R_2 = R_3 = 10 k\Omega$

QUESTION (5)

The following is a single stage common source amplifier circuit.

Given: $V_{TH} = 1\text{ V}$, $K = 4\text{ mA/V}^2$, and $\lambda = 0$

- For a supply voltage $V_{DD} = 15\text{ V}$, design the bias circuit such that $I_D = 0.5\text{ mA}$, $V_S = 3.5\text{ V}$, and $V_D = 6\text{ V}$. Please specify the values for R_{G1} , R_{G2} , R_S and R_D . (10 points)
- Assuming that the equivalent input resistance $R_{in} = 1.67\text{ M}\Omega$, $R_1 = 100\text{ k}\Omega$, $R_L = 200\text{ k}\Omega$, determine the overall small signal voltage gain v_1/v_{out} . (10 points)

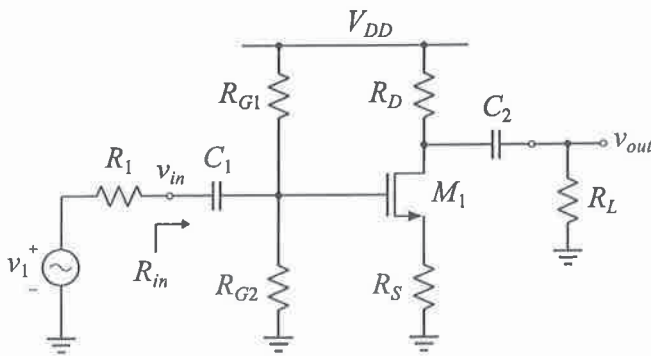

Useful formulae: for n-channel MOSFET

$$i_{DS} = K \left[(v_{GS} - V_{TH})v_{DS} - \frac{1}{2}v_{DS}^2 \right] \quad \text{triode region}$$

$$i_{DS} = \frac{1}{2}K (v_{GS} - V_{TH})^2 (1 + \lambda v_{DS}) \quad \text{saturation region}$$