

# National Exams December 2018

## 17-Comp-A1, Electronics

3 hours duration

### **NOTES:**

1. If doubt exists as to the interpretation of any question, the candidate is urged to indicate, with the answer, a clear statement of any assumptions made.
2. This is an OPEN BOOK exam.  
Any non-communicating calculator is permitted.
3. FIVE (5) questions constitute a complete exam paper.  
The first 5 questions as they appear in the answer book will be marked.
4. Each question is of equal value.

### Marking Scheme

1. 20 marks total (4 parts, 5 marks each)
2. 20 marks total (4 parts, 5 marks each)
3. 20 marks total (4 parts, 5 marks each)
4. 20 marks total (4 parts, 5 marks each)
5. 20 marks total (4 parts, 5 marks each)
6. 20 marks total (4 parts, 5 marks each)
7. 20 marks total (4 parts, 5 marks each)

 
**Question 1 (20 marks)**

Figure 1. All diodes have a forward voltage drop  $V_D=0.7V$ .

The circuit shown in Figure 1 is in steady state:

- Sketch  $V_s$  and  $V_o$  as a function of time, indicating peak voltages.
- Sketch  $V_R$  as a function of time, indicating peak voltages.
- Which resistor has the largest peak power dissipation? What power rating would you choose for this resistor?
- Sketch current  $I_s$  as a function of time, indicating peak values.

 
**Question 2 (20 marks)**

Figure 2.  $I=500 \mu\text{A}$ ,  $k_n'(W/L)=3k_p'(W/L)=1 \text{ mA/V}^2$ ,  $V_{tn}=|V_{tp}|=1.0\text{V}$ ,  $V_A=80\text{V}$

For the circuit shown in Figure 2:

- Draw a small signal AC equivalent circuit and find the model parameter values.
- Find the input and output resistances of the circuit.
- Find the open circuit voltage gain for the amplifier.
- If the output drives a  $50\Omega$  load, what is the voltage gain?

**Question 3 (20 marks)**

 


Figure 3. The operational amplifier saturates at  $\pm 10\text{V}$ . The DC input bias current in each input terminal is  $10\ \mu\text{A}$ .

For the circuit shown in Figure 3:

- Find the circuit AC gain.
- Sketch the frequency response of the circuit.
- Find the 3dB frequencies, bandwidth and passband gain for this circuit.
- What is the effect of the input bias current on output voltage offset?

**Question 4(20 marks)**

 


Figure 4.  $I=1\text{mA}$ ,  $\beta=100$ ,  $V_A=100\text{V}$ ,  $V_T=25\text{mV}$ .

For the circuit shown in Figure 4:

- Find  $V_C$ ,  $V_B$  and  $V_E$ .
- Draw a small signal equivalent circuit and find the model parameter values.
- Find the small signal input resistance  $R_i$  and output resistance  $R_o$ .
- Find the open circuit voltage gain for the amplifier and the loaded voltage gain.

**Question 5 (20 marks)**

 


Figure 5.  $R_1=R_4=1k\Omega$ ,  $R_2=R_3=10k\Omega$ ,  $C_1=C_2=1nF$

For the circuit shown in Figure 5:

- Explain operation of the circuit.
- Where would you take the circuit output?.
- For the component values given, at what frequency would the circuit operate ?
- Select new component values to provide a duty cycle of 66% at the same operating frequency.

**Question 6 (20 marks)**

Consider a CMOS technology in which an inverter with a minimum gate length  $L=0.5 \mu\text{m}$  has a symmetric transfer function for NMOS  $W/L = 1.5$  and PMOS  $W/L = 6$ .

- a) Sketch the transistor level gate schematic for the Boolean function  
$$Y = \overline{(AB + C)}D.$$
- b) Specify sizes ( $W/L$ ) for all transistors in order to achieve current-driving capability equal to that of the basic inverter.
- c) Repeat a) and b)  $Y = A\overline{B} + \overline{A}B.$
- d) For the gate in c), find the ratio of maximum to minimum available current to charge and discharge a load.

**Question 7 (20 marks)**

 


Figure 6.  $V_{REF}$  is a positive reference. The capacitor is initially discharged.  
 $R=10k\Omega$ ,  $C=10\mu F$ ,  $V_{IN}=-2V$ ,  $V_{REF}=2.5V$

- a) For a DC input  $V_{IN}$ , sketch  $V_x(t)$ .
- b) Find the slope of  $V_x(t)$ .
- c) A counter with a clock of 1MHz stops when  $V_{OUT}$  goes high. What is the counter value?
- d) What are the applications and limitations of this circuit?