

**PROFESSIONAL ENGINEERS ONTARIO**

**National Examinations - May 2013**

**07-Mec-A5, Electrical & Electronics Engineering**

**Mechanical Engineering**

3 hours duration

---

Name [print]:

Signature:

---


Notes:

- [1] If doubt exists as to the interpretation of any question, the candidate is urged to submit, with the answer paper, a clear statement of any assumptions made.
- [2] Candidates may use one of two calculators, the Casio or Sharp approved models. This is a closed book examination.
- [3] This examination consists of the front page and 8 numbered pages.
- [4] Any five (5) questions constitute a complete paper. Only the first five questions as they appear in your answer book will be marked.
- [5] Each question is of equal value.
- [6] Clarity and organization of answers are important.
- [7] The candidate is required to sign this examination paper and submit it with the solution booklets.
- [8]  $\pi = 3.14159$   
 $1 \text{ hp} = 746 \text{ W}$   
 $\mu_0 = 4\pi \times 10^{-7} \text{ H m}^{-1}$

**QUESTION 1**

Consider the transistor circuit shown in Figure 1. All transistors can be assumed to be identical with a dc current gain  $\beta$ .

Calculate the current transfer ratio for the circuit,  $I_2 / I_1$ , as a function of  $\beta$ .

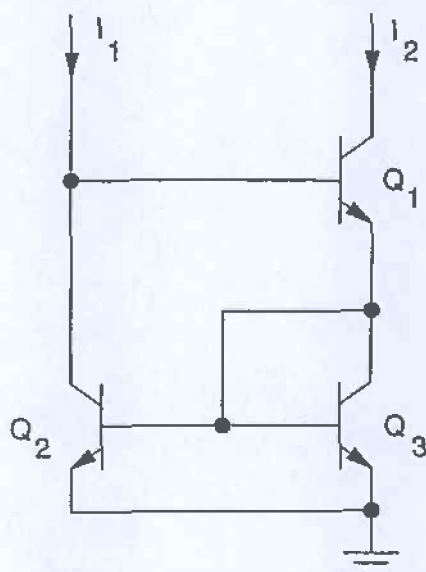

**Figure 1 Transistor Circuit**

## QUESTION 2

This question consists of two parts which are not necessarily related.

### Part I

A combinational logic circuit is shown in Figure 2.

- Write a general Boolean algebra expression for the output F as a function of the inputs A, B.
- Using DeMorgan's theorems and other Boolean identities, simplify the expression obtained in [a]. Is there a single gate which can replace the network shown?
- Generate a truth table giving the logic levels at points C, D, E and F for inputs A,B.

### Part II

Design a 2-input exclusive or (EOR) gate using only 2-input NOR gates.

- Develop the truth table for the gate.
- Write a general Boolean algebra expression for the output as a function of the inputs.
- Using DeMorgan's theorems and other Boolean identities, modify the expression obtained in [e] to provide a solution which can be implemented with NOR gates.
- Draw the circuit diagram for the final gate array.

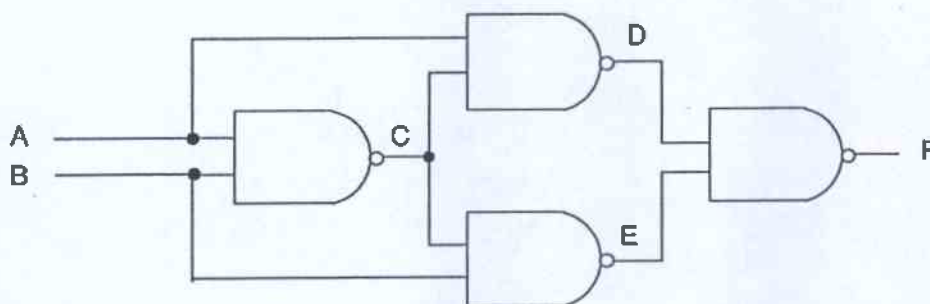



Figure 2 Combinational Logic Circuit

**QUESTION 3**

A novel type of DC machine is designed using a disc type rotor of effective outer and inner diameters  $D$  and  $d$  respectively, as shown in Figure 3. A current  $I_2$  is fed radially through the rotor via two ring shaped carbon brushes. The rotor lies in the horizontal plane and is situated in a vertical magnetic field of uniform density,  $B$  Tesla. The rotor spins at an angular speed  $\omega$  rad/s.

- [a] Find the magnitude of the emf  $e$  generated between the brushes.
- [b] Determine the torque that the rotor will be subjected to and find the output horsepower of the machine.

**HINT:** As a starting point, consider an elemental annulus of radius  $r$  and radial length  $dr$ .

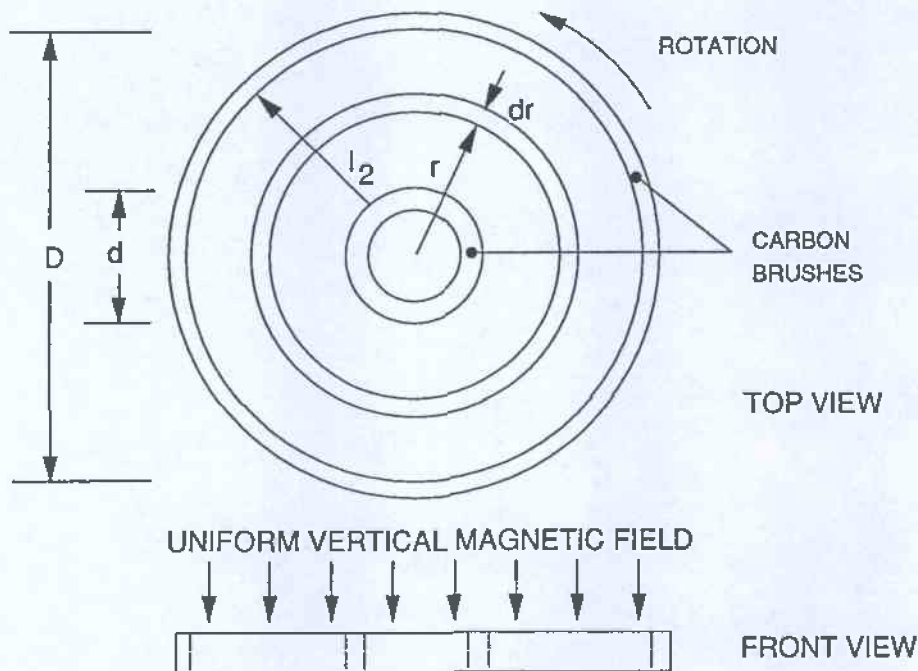

**Figure 3 dc Machine**

## QUESTION 4

An industrial load is represented in Figure 4 by  $R = 6\Omega$  and  $X_L = 8\Omega$ . The load voltage is  $250\angle 0^\circ$  V.

- Calculate the load current, power, reactive power and power factor.
- Calculate the generator voltage  $V_G$  required at the input end of the transmission line (represented by the series impedance  $Z_T = (1 + j3)\Omega$ ) and the power lost in transmission  $P_T$ .
- If capacitor  $X_C = 12.5\Omega$  is connected in parallel by closing switch S, calculate  $I_C$ , the new load current I, and the new power factor. Show V,  $I_L$ ,  $I_C$ , and I on a phasor diagram.
- Calculate the new generator voltage and the new transmission power loss.
- What two advantages do you see for improving the power factor by adding a parallel capacitor?

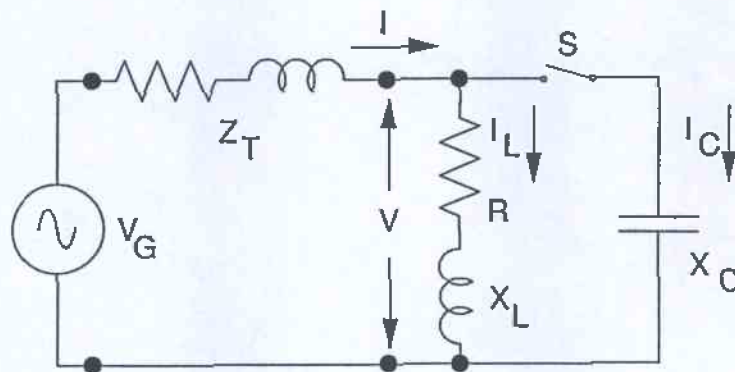


Figure 4 Industrial Load

### QUESTION 5

Consider the circuit shown in Figure 5 which has been designed using ideal operational amplifiers ( $U_1$  to  $U_3$ ) with infinite bandwidth and infinite open loop gain. In the schematic,  $a$ ,  $b$  and  $c$  are constants. You will note that  $U_3$  is configured as a basic difference amplifier which has a transfer function given by:

$$E_0 = c (e_y - e_x)$$

where  $e_y$  and  $e_x$  are the potentials at points  $y$  and  $x$  respectively.

In the derivation of the transfer function for such circuits, one can assume:

- [i] Zero differential voltage between the input terminals of the operational amplifier,
- [ii] Zero current flows into either input terminal of the operational amplifier.

Applying the principle of superposition, derive an expression for the transfer function of the total circuit [ $E_0$  as a function of  $E_1$ ,  $E_2$ ].

**Hint:** Let  $E_2 = 0$ , and solve for the potentials at points  $x$  and  $y$  for input  $E_1$ .  
Let  $E_1 = 0$ , and again solve for the potentials at points  $x$  and  $y$  for input  $E_2$ .  
Calculate the resultant output  $E_0$  for both  $E_1$  and  $E_2$  inputs.

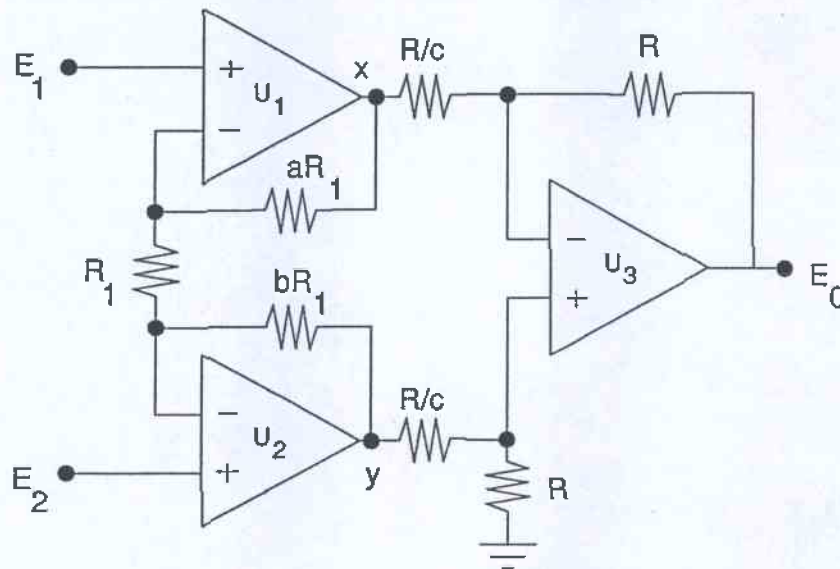


Figure 5 Circuit Schematic

**QUESTION 6****Part I**

A dc test is performed on a 208-V, six-pole, delta connected, 60Hz induction motor, as shown in Figure 6.

[a] If  $V_{DC} = 3.32$  V and  $I_{DC} = 3.1$  A, calculate the per phase stator resistance,  $r_1$ .

Three phase excitation is applied to the motor which runs with a slip of 3.5%. Find:


- [b] The speed of the magnetic field in revolutions per minute.
- [c] The speed of the rotor in revolutions per minute.
- [d] The electrical frequency of the rotor current.

The load on the motor is now doubled. Calculate:

- [e] The speed of the rotor in revolutions per minute.

**Part II**

You are provided with a graph of the speed-torque characteristic of a three phase wound rotor induction motor. The torque required to drive a pump is  $T = K_p n^2$  ( $K_p$  is a constant;  $n$  is speed in revolutions/second). The induction motor is to be used to drive the pump. Show how you would determine the operating point speed of the system.

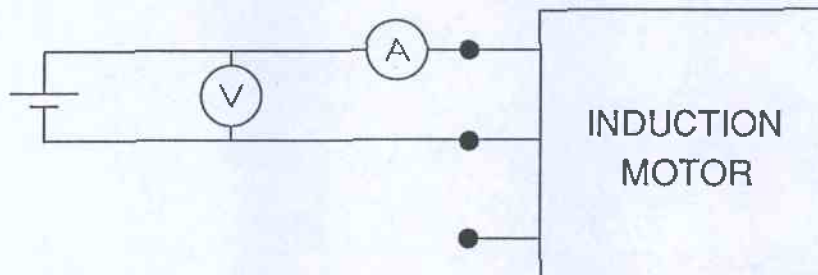

**Figure 6 dc Test on Induction Motor**


**QUESTION 7**

Consider the RC circuit shown in Figure 7[a]. The switch  $S_1$  is closed at time  $t=0$  connecting the dc supply  $V_1$  to the network.


- [a] Derive an expression for the transfer function of the circuit,  $V_o/V_1$ , in the time domain.
- [b] Sketch the transfer function for a time interval of 5 time constants.

The RC circuit is reconfigured as shown in Figure 7[b]. An ac voltage source of variable frequency  $v_i$  is connected to the input.

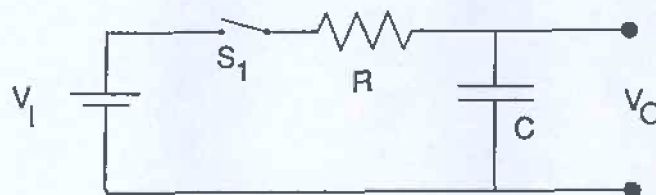- [c] Derive an expression for the transfer function of the circuit,  $v_o/v_i$ , in the frequency domain.
- [d] Sketch the magnitude of the transfer function for a frequency range of 4 decades centered at the corner frequency of the circuit.



[a]

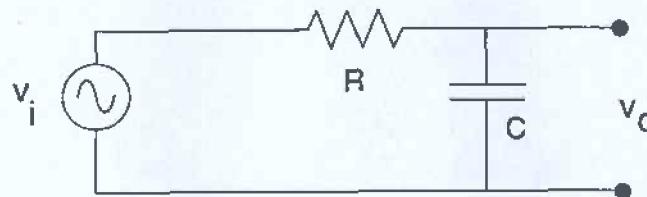

[b]

**Figure 7 RC Circuit: [a] dc test; [b] ac test**




**QUESTION 8**

Consider the magnetic circuit shown in Figure 8. An ac voltage source  $v_1(t)$  is applied to the primary winding, with  $N_1$  turns, which results in a primary current  $i_1(t)$ . A voltmeter is used to measure the voltage induced in the secondary winding  $v_2(t)$ . The magnetic circuit has a mean length of  $L$  m, a cross sectional area of  $A$  m<sup>2</sup> and a relative permeability of  $\mu_r$ . The primary current is given by:

$$i_1(t) = I_p \sin \omega t$$

where  $I_p$  is the peak value of the primary current and  $\omega$  is the radian frequency of the supply voltage source. Neglect the resistance of the windings, leakage inductances and other losses.

- [a] Develop expressions for the primary voltage  $v_1(t)$  and the secondary voltage  $v_2(t)$  as a function of the current  $i_1(t)$ .
- [b] Develop an expression for the impedance of this circuit as viewed from the primary.
- [c] Sketch waveforms for the primary voltage  $v_{AB}$  and the secondary voltage  $v_{XY}$  showing the magnitudes and phase relations with respect to the primary current  $i_1(t)$ .

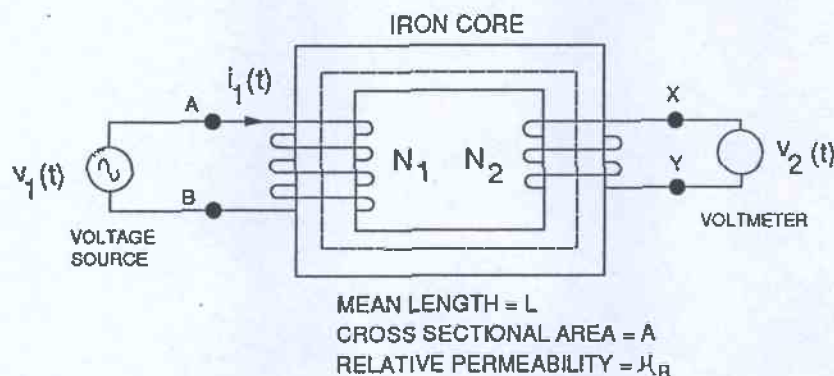

**Figure 8 Magnetic Circuit**