

National Exam May 2018

16-Elec-A1, Circuits

3 hours duration

NOTES:

1. **No questions to be asked.** If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any logical assumptions made.
2. **One of two calculators is permitted - any Casio or Sharp approved model. No programmable models** are allowed.
3. This is a **closed book** examination.
4. Any **five questions** constitute a complete paper. Please **indicate in the front page of your answer book which questions you want to be marked.** If not indicated, only the first five questions as they appear in your answer book will be marked.
5. All questions are of equal value. **Part marks will be given for right procedures.**
6. **Some useful equations and transforms** are given in the last page of this question paper.

Q1:(a) In the circuit shown in Figure-1, calculate the equivalent resistance at terminals a-b, R_{ab} . [10]

(b) Calculate the current, I_0 as shown in the circuit. [10]

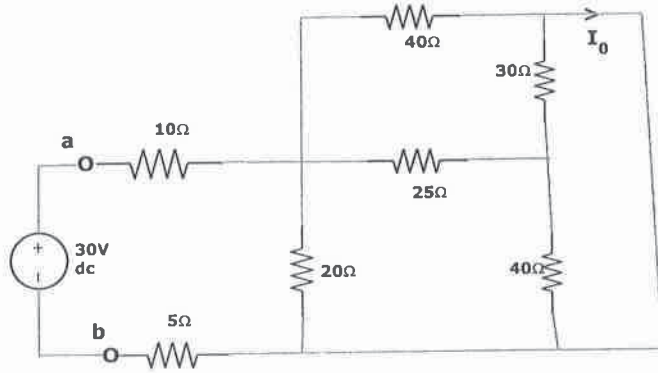


Figure-1

Q2: (a) Write the Node Voltage equations of the circuit shown in Figure-2. [9]

(b) Solve the Node Voltages. [6]

(c) Solve V_o in the circuit. [5]

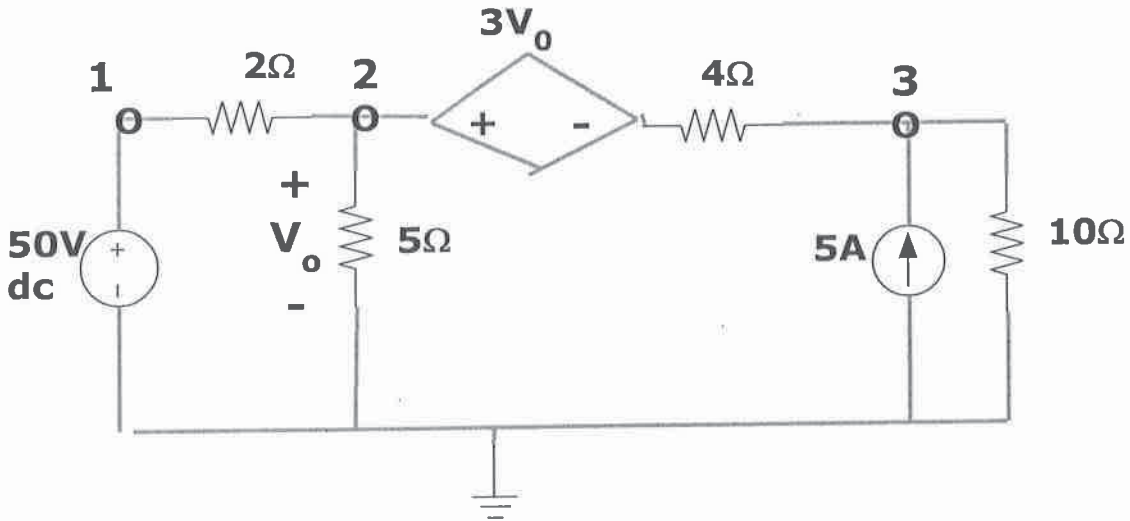


Figure-2

Q3: For the Circuit shown in Figure-3, the switch was initially closed for a long time.

At $t=0$, the switch is opened.

- (a) Solve $V_c(0^+)$ i.e just after the switch was opened. [2]
- (b) Solve $\frac{dv_c}{dt}(0^+)$ [4]
- (c) Solve $V_c(t)$, $t \geq 0$ [10]
- (d) Sketch $V_c(t)$ for $t \geq 0$ [4]

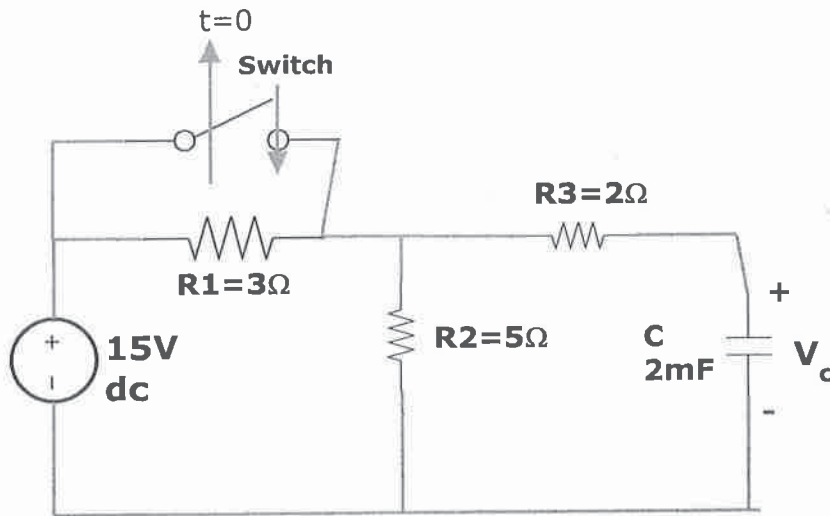


Figure-3

- Q4: (a) Transform the circuit in Figure-4 from time domain to phasor domain [5]
- (b) Write the mesh current equations of the circuit [8]
- (c) Solve V_0 in phasor, and in time domain, $V(t)$ [5+2]

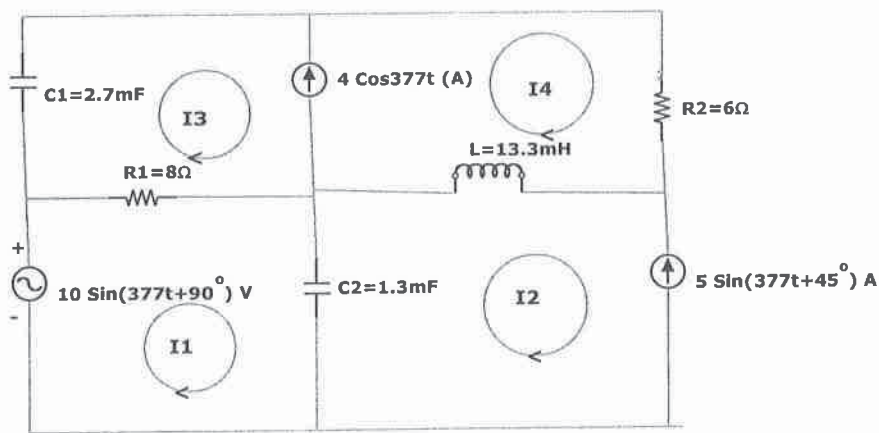


Figure-4

- Q5:** (a) Calculate the Thevenin's Voltage, V_{th} and Thevenin's impedance, Z_{th} at the terminals **a-b** of the circuit shown in Figure-5. [6+6]
 (b) What value of load impedance Z_L which can be connected at terminals **a-b** for maximum power dissipation in Z_L ? [2]
 (c) Calculate the maximum power, P_{max} which can be dissipated in Z_L . [6]

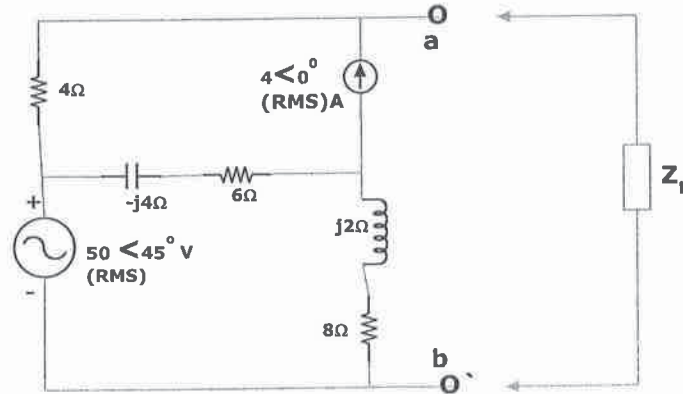


Figure-5

Q6: In the circuit shown in Figure-6, input voltage of 15V dc was switched ON at $t=0$.

- (a) Convert the circuit its Laplace equivalent at $t > 0$, if $i_L(0^-) = 2A$ and $v_c(0^-) = 6V$. [5]
 (b) Find the capacitor voltage, $V_c(s)$ in the frequency domain. [5]
 (c) Solve $V_c(t)$ in the time domain. [10]

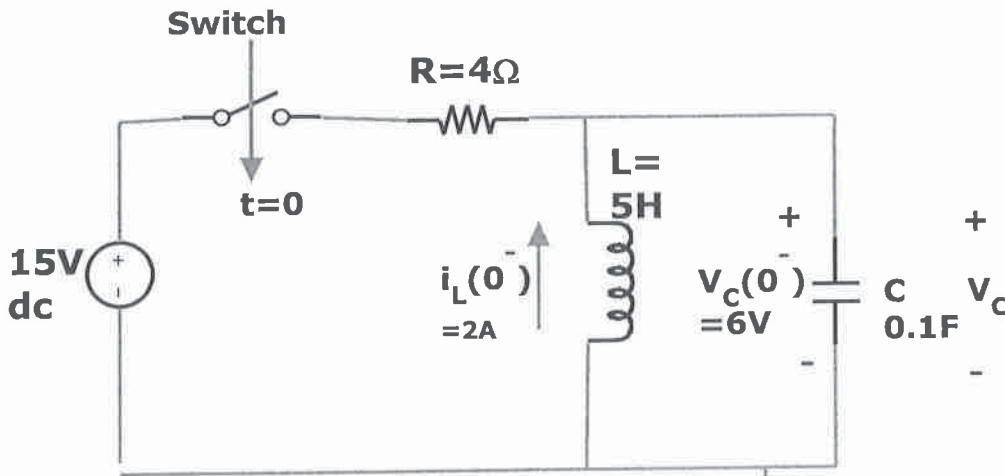
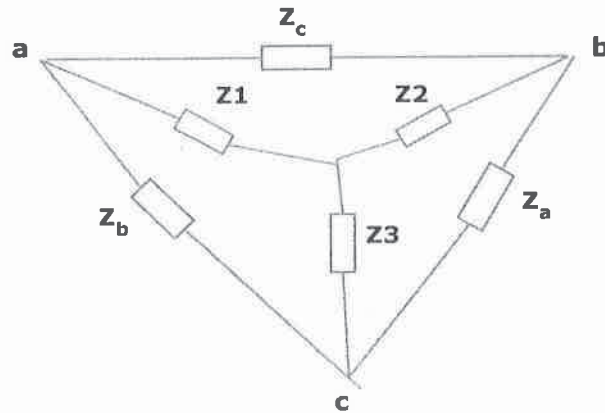


Figure-6

Appendix

Some useful Laplace Transforms:

<u>f(t)</u>	→	<u>F(s)</u>
$Ku(t)$		K / s
$\delta(t)$		1
t		$1/s^2$
$e^{-at} u(t)$		$1 / (s+a)$
$\sin \omega t \cdot u(t)$		$\omega / (s^2+\omega^2)$
$\cos \omega t \cdot u(t)$		$s / (s^2+\omega^2)$
$e^{-at} \sin \omega t$		$\frac{\omega}{(s+\alpha)^2+\omega^2}$
$e^{-at} \cos \omega t$		$\frac{(s+\alpha)}{(s+\alpha)^2+\omega^2}$
$\frac{df(t)}{dt}$		$s F(s) - f(0^-)$
$\frac{d^2 f(t)}{dt^2}$		$s^2 F(s) - s f(0^-) - f'(0^-)$
$\int_{-\infty}^t f(q) dq$		$\frac{F(s)}{s} + \int_{-\infty}^0 f(q) dq$

Star – Delta conversion:

$$Z_1 = \frac{Z_b \cdot Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a \cdot Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a \cdot Z_b}{Z_a + Z_b + Z_c}$$

$$Z_a = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_3}$$

$$Z_b = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_1}$$