

## National Exams May 2014

07-Elec-A5, Electronics

3 hours duration

### Notes:


1. If any doubt exists as to the interpretation of any question, the candidate is urged to submit, within their answer, a clear statement of any assumptions made.
2. This is a **CLOSED BOOK EXAM**.  
Any non-communicating calculator is permitted.
3. Answer all **FIVE** (5) questions.
4. All questions are worth 20 marks each.
5. Please start each question on a new page and clearly identify the question number and part number, e.g. Q4(a).
6. In schematics, ground and chassis may be assumed to be common, unless specifically stated otherwise.
7. Unless otherwise specified, assume that Op-Amps are ideal and that supply voltages are  $\pm 15V$ .
8. If questions require an answer in essay format, clarity and organization of the answer are important. Provide block diagrams and circuit schematics whenever necessary.

**QUESTION (1)**

The op amp in this circuit is ideal except for an input bias current of 100nA in each of the input terminal.

Given  $C_1 = \infty$ , design this circuit to meet the following specifications:

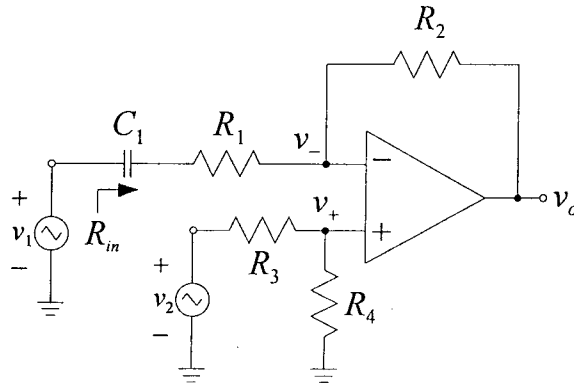- a)  $v_o = v_2 - v_1$
- b)  $R_{in} = 1 \text{ M}\Omega$
- c) Minimum output offset voltage



Provide values for  $R_1, R_2, R_3$  and  $R_4$ .

(20 points)

**QUESTION (2)**

The p-channel MOSFET,  $M_1$  in this circuit has the following characteristics:


$$|V_{TH}| = 1 \text{ V}$$

$$K = 2 \text{ mA/V}^2 \quad \lambda = 0.01 \text{ V}^{-1}$$

Given:

$$V_{DD} = 10 \text{ V} \quad R_L = R_S = 2 \text{ k}\Omega$$

$$C_1 = C_2 = \infty$$

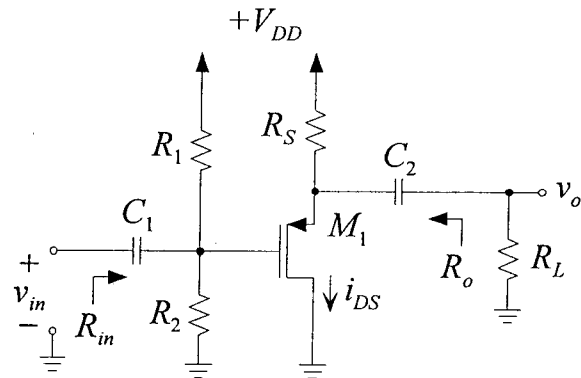

- a) Design this circuit to have the following specifications:

$$R_{in} = 100 \text{ k}\Omega, I_{SD} = 2 \text{ mA}$$

Provide values for  $R_1$ , and  $R_2$ . (8 points)

- b) Determine the output resistance,  $R_o$ .

(6 points)

- c) Determine the maximum undistorted peak to peak output voltage?


(6 points)

Useful formulae: for p-channel MOSFET

$$i_{SD} = K \left[ 2(v_{SG} - |V_{TH}|)v_{SD} - v_{SD}^2 \right] \quad \text{triode region}$$

$$i_{SD} = K (v_{SG} - |V_{TH}|)^2 (1 + \lambda v_{SD}) \quad \text{saturation region}$$

**QUESTION (3)**

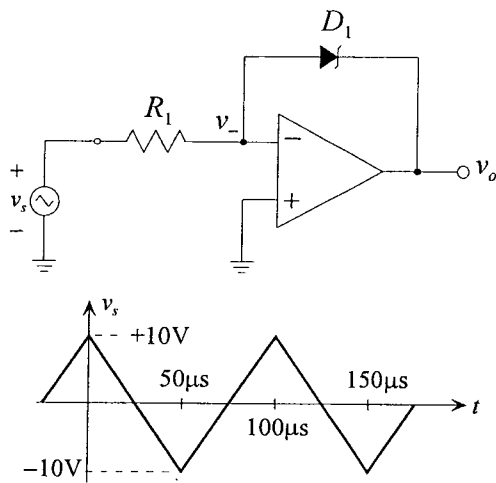


The op amp in this circuit is ideal except for a slew rate limit of  $0.5\text{V}/\mu\text{s}$ . It is powered by  $\pm 15\text{V}$  supplies. Given that

$$R_1 = 10\text{k}\Omega$$

For  $D_1$ ,  $V_Z = 5\text{V}$ , forward voltage drop =  $0.7\text{V}$

Sketch **accurately** in your answer book the voltage waveform for  $v_o$ . You must indicate the breakpoints, including the accurate timing and voltage levels. (20 points)

**QUESTION (4)**

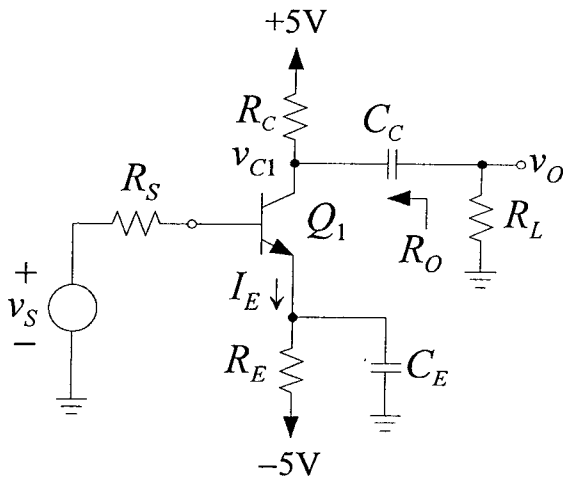

The BJT,  $Q_1$  has the following characteristics:

$$\beta = 100$$

$$V_{BE(\text{on})} = 0.7\text{V}$$

$$V_{CE(\text{sat})} = 0.3\text{V}$$

$$V_A = \infty$$

$$R_S = 100\Omega$$

$C_E$ , and  $C_C$  are large capacitors

- Design this common collector amplifier circuit to have an open circuit gain (i.e. without  $R_L$ ) of  $100\text{V}/\text{V}$  with a DC bias current,  $I_E = 2\text{mA}$ . Provide values for  $R_E$  and  $R_C$ . (8 points)
- What is the equivalent output resistance,  $R_O$ ? (6 points)
- For a  $1\text{mV}$  peak to peak sine wave input at  $1\text{kHz}$ , sketch accurately the waveforms at the collector of  $Q_1$ ,  $v_{C1}$  and at the output  $v_o$ . Remember to take into account the fact that  $R_L = 1.25\text{k}\Omega$ . (6 points)

**QUESTION (5)**

In the following circuits, assume that the diode is ideal and has a forward voltage of 0.7V. Sketch the output waveform for one complete sine wave input. (20 points)

