

National Exams May 2019

**17-Phys-A5-B Analog and Digital Electronic Circuits**

3 hours duration

**NOTES:**

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any assumptions made.
2. This is an OPEN BOOK EXAM.  
Any non-communicating calculator is permitted.
3. Answer all SIX (6) questions.
4. Please start each question on a new page and clearly identify the question number and part number, e.g. Q1(a).
5. If questions require an answer in essay format, clarity and organization of the answer are important. Provide block diagrams and circuit schematics whenever necessary.

**Marking Scheme**

1. 15 marks
2. (a) 10 marks; (b) 10 marks;
3. (a) 10 marks; (b) 10 marks
4. 15 marks
5. (a) 10 marks; (b) 5 marks
6. 15 marks

**Question 1**

For the circuit, shown in Fig.1, assume the diode has a 0.7 V drop when conducting.

- (a) Find the output voltage  $v_o$  in terms of the input  $v_{in}$  and sketch clearly  $v_o$  versus  $v_{in}$  when  $v_{in}$  changes over the range of  $\pm 8V$ . Mark on the plot the values of  $v_o$  for  $v_{in} = \pm 8V$ .

 


Fig.1

**Question 2**

In the circuit in Fig.2, assume  $Q_1$  has  $\beta = 50$  and  $V_{EB} = 0.7V$  for the dc analysis and neglect Early effect ( $V_A = \infty$ ).

- (a) Find the dc current  $I_c$ .  
 (b) Calculate the input resistance  $R_i$ .

 


Fig.2

**Question 3**

For the MOS circuit shown in Fig. 3, consider  $I_{bias}$  is an ideal current source,  $V_b$  is a constant dc voltage,  $g_{m1} \neq g_{m2} \neq g_{m3} \neq g_{m4}$ , and  $r_{o1} \neq r_{o2} \neq r_{o3} \neq r_{o4} \neq \infty$ . Assume all the transistors are in active region.

- (a) Find the expression of the differential gain  $A_d = |v_o/v_{id}|$ .
- (b) Find the 3-dB frequency,  $f_H$ , of the differential gain  $A_d = |v_o/v_{id}|$  while including the parasitic capacitances  $C_{GS}$  for all transistors.

 


Fig. 3

**Question 4**

For the amplifier in Fig. 4 assume that  $g_{m1} = g_{m2} \neq g_{m3}$ , and  $r_{o1} = r_{o2} = r_{o3} = \infty$ .  $I_{bias}$  is an ideal current source. Assume all transistors are in saturation region.

 


Fig. 4

- (a) Use the methods of feedback analysis to find the expression of the gain  $v_o/v_s$ .

### Question 5

Consider the 3-bit digital-to-analog converter (DAC) using an R-2R resistive ladder as shown in Fig. 5. Assume an ideal Op-Amp.

 


Fig. 5

- (a) Find the expressions of the output voltage  $V_o$   
 (b) Calculate  $V_o$  when  $R = 10\text{k}\Omega$ ,  $V_{REF} = 5\text{ V}$  and the applied binary word is  $S_2S_1S_0 = 101$ .

### Question 6

Implement the logic function  $Y = A \cdot B \cdot C + D$  using static CMOS logic gate with NMOS and PMOS transistors. Mark on the schematic clearly the pull-down network (PDN) and the pull-up network (PUN) that implements the function  $Y$ .