

National Exams May 2019

17-Comp-A1, Electronics

3 hours duration

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate is urged to indicate, with the answer, a clear statement of any assumptions made.
2. This is an OPEN BOOK exam.
Any non-communicating calculator is permitted.
3. FIVE (5) questions constitute a complete exam paper.
The first 5 questions as they appear in the answer book will be marked.
4. Each question is of equal value.

Marking Scheme

1. 20 marks total (4 parts, 5 marks each)
2. 20 marks total (3 parts, a)7 marks, b)7 marks, c) 6 marks)
3. 20 marks total (4 parts, 5 marks each)
4. 20 marks total (4 parts, 5 marks each)
5. 20 marks total (3 parts, a) 6 marks, b) 7marks, c) 7 marks)
6. 20 marks total (4 parts, 5 marks each)
7. 20 marks total (4 parts, 5 marks each)

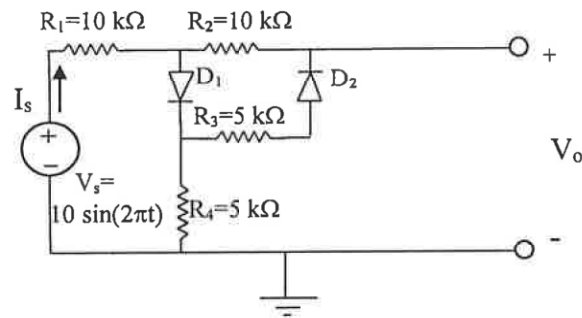
Question 1 (20 marks)

Figure 1. All diodes have a forward voltage drop $V_D=0.7V$.

The circuit shown in Figure 1 is in steady state:

- Sketch V_s and V_o as a function of time, indicating peak voltages.
- What maximum reverse voltage rating would you choose for the diodes?
- Which resistor has the largest peak power dissipation? What power rating would you choose for this resistor?
- Sketch current I_s as a function of time, indicating peak values.

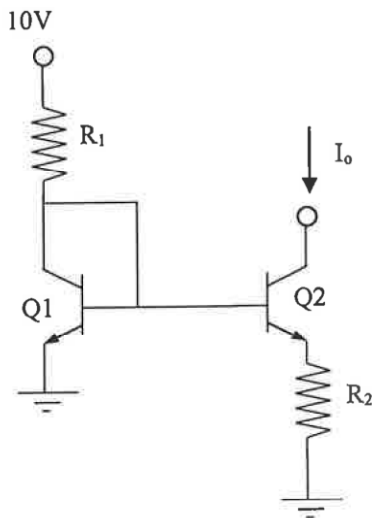
Question 2 (20 marks)

Figure 2. $V_{BE}=0.7V$ for $I_C=1mA$, $\beta=100$, $V_T=25mV$, $V_A=100V$.

For the circuit shown in Figure 2:

- Choose R_1 and R_2 so I_o is $100 \mu A$
- Find the small signal output resistance of the circuit.
- If $R_2=0\Omega$, repeat a) and b).

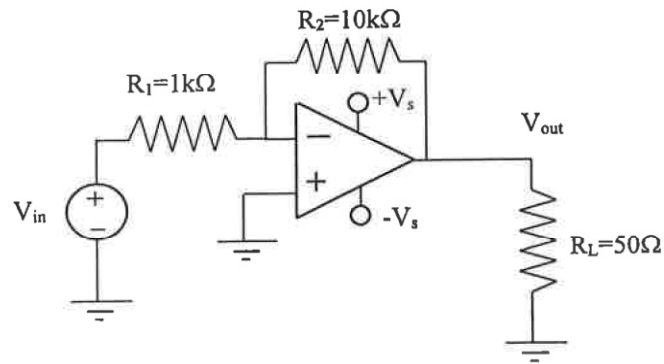
Question 3 (20 marks)

Figure 3. $+V_s=15\text{V}$, $-V_s=-15\text{V}$, $I_s=100\text{mA}$ from each supply, $V_{in}=1\text{V}@1\text{kHz}$.

For the circuit shown in Figure 3:

- Find voltage gain $|A_v|$ and power gain $|A_p|$ in dB
- Find the efficiency of the amplifier
- Draw an equivalent circuit for the amplifier including component values
- What is the maximum input possible without clipping of the output waveform?

Question 4(20 marks)

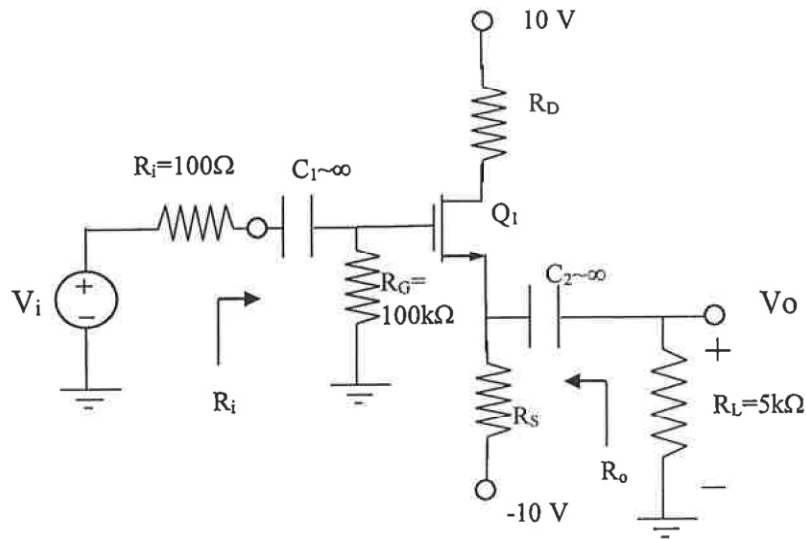


Figure 4. $k_n'(W/L)=0.5\text{mA/V}^2$, $V_t=2\text{V}$, $V_A=50\text{V}$

For the circuit shown in Figure 4:

- Choose values for R_D and R_S to provide $I_D=1\text{mA}$.
- Draw a small signal equivalent circuit and evaluate the model parameter values.
- Find the small signal input resistance R_i and output resistance R_o .
- Find the voltage gain for the amplifier.

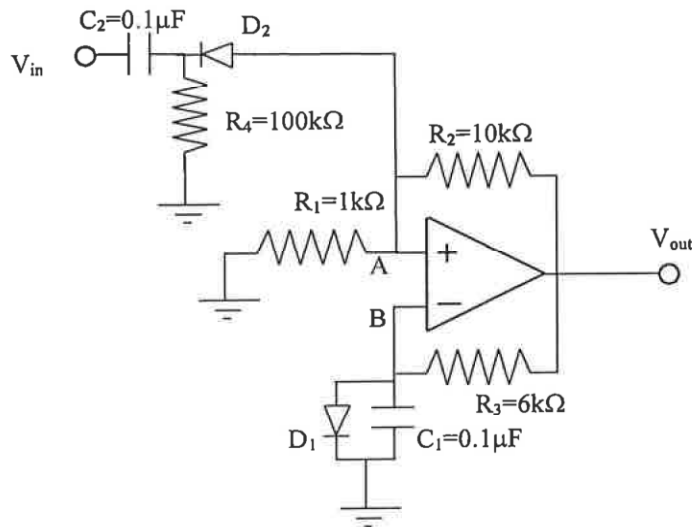
Question 5 (20 marks)

Figure 5.

The circuit shown in Figure 5 is in steady state with $V_{in}=0\text{V}$ for $t<0$. At $t=0$ V_{in} drops to -5V . All diodes have a forward voltage drop $V_D=0.7\text{V}$. The amplifier is supplied $\pm 12\text{V}$.

- For $t<0$ explain the expected steady state value for V_{out} .
- For $t>0$ explain the circuit operation
- For $t>0$ sketch V_{out} , V_A and V_B as a function of time including key amplitude and time values.

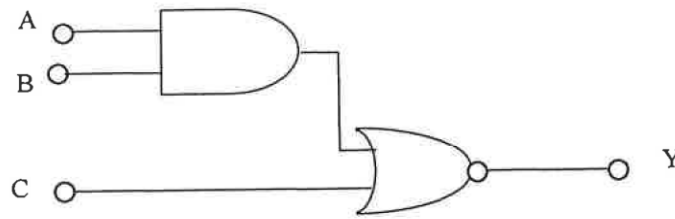
Question 6 (20 marks)

Figure 6.

Consider a CMOS technology with $C_{ox}=1\text{fF}/\mu\text{m}^2$, $\mu_n C_{ox}=50\mu\text{A}/\text{V}^2$, $\mu_p C_{ox}=20\mu\text{A}/\text{V}^2$, $V_{tn}=-V_{tp}=1\text{V}$, and $V_{DD}=5\text{V}$. An inverter with a minimum gate length $L=0.5\mu\text{m}$ has a symmetric transfer function for NMOS $W/L = 1.5$ and PMOS $W/L = 6$.

- Provide a Boolean expression for Y based on the gate combination shown in Figure 6.
- Synthesize a transistor level CMOS logic circuit to implement this expression.
- Specify sizes (W/L) for all transistors in order to achieve current-driving capability equal to that of the basic inverter.
- If the output Y drives a standard inverter in this technology, evaluate the propagation delays considering only the inverter gate capacitance as a load.

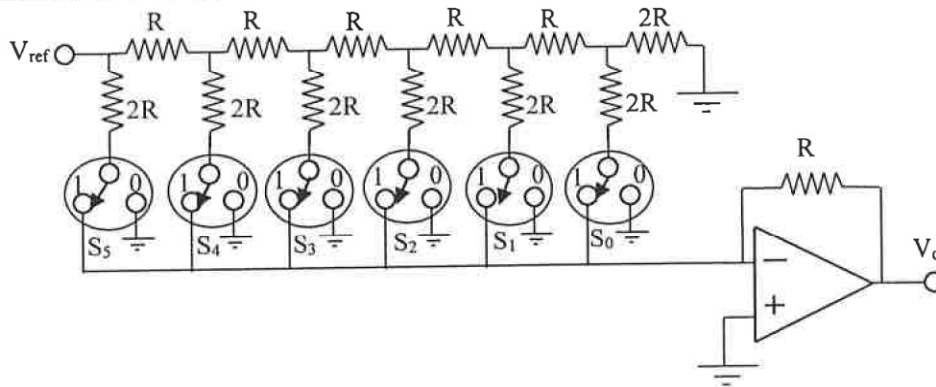
Question 7 (20 marks)

Figure 7. $R=10k\Omega$, $V_{REF}=2.5V$. Switches hold the position shown if the control voltage is high, and connect to ground if the control voltage is low.

- Evaluate the current through each switch if the control signal $S=(111111)$
- Evaluate the current through each switch if the control signal $S=(000000)$
- Evaluate the output voltage for $S=(001001)$.
- Describe another approach to implement the function of this circuit.