

National Exam, May 2019

16-Elec-A1 Circuits

3 hours duration

NOTES:

1. **No questions to be asked.** If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any logical assumptions made.
2. One of two calculators is permitted – any Casio or Sharp approved model.
3. This is a **closed book** examination.
4. Any **five questions** constitute a complete paper. Please **indicate in the front page of your answer book which questions you want to be marked.** *If not indicated, only the first five questions as they appear in your answer book will be marked.*
5. All questions are of equal value. **Part marks will be given for right procedures.**
6. **Some useful equations and transforms** are given in the last page of this question paper.

Q1: For the circuit shown in Figure-1,

- (a) Calculate the equivalent resistance of the circuit, R_{AB} at the terminals A and B. [10]
- (b) Solve for the current I_1 at the location shown. [5]
- (c) Calculate current I_2 through the 3Ω resistance. [5]

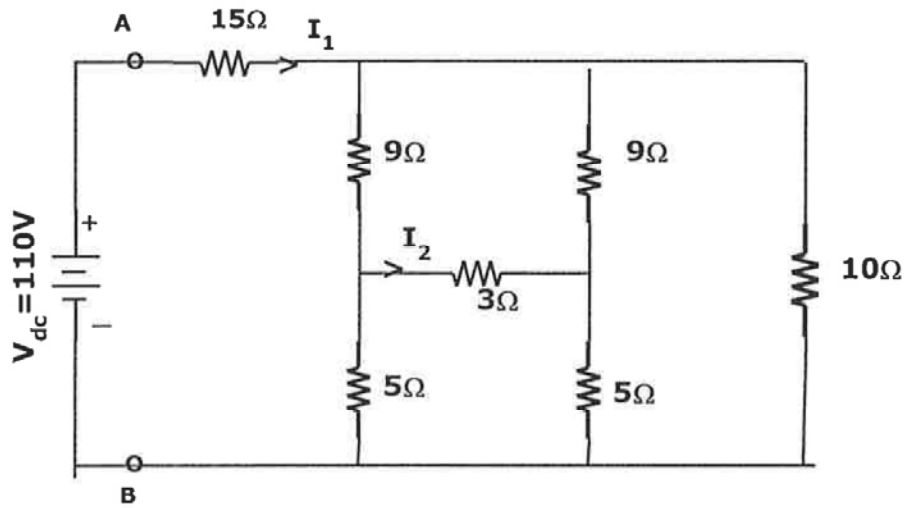


Figure-1

Q2: In the circuit shown in Figure-2,

- (a) Write the node voltage equations for V_1 , V_2 and V_3 . [10]
- (b) Solve the node voltages. [10]

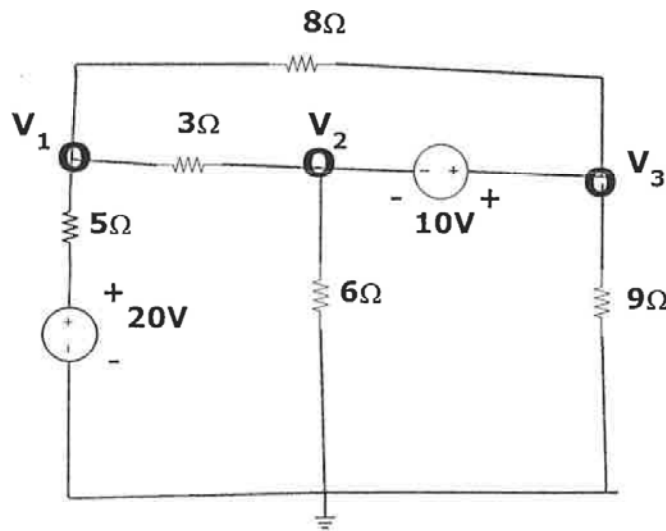


Figure-2

Q3: In Figure-3, the switch was in position-a for a long time. At $t = 0$, it is moved to Position-b.

- Calculate (i) $v_c(0+)$, $\frac{dv_c}{dt}(0+)$, $i_c(0+)$ and $v_c(\infty)$ [4+4+2+2]
 (ii) $v_c(t)$ when $t \geq 0$ [8]

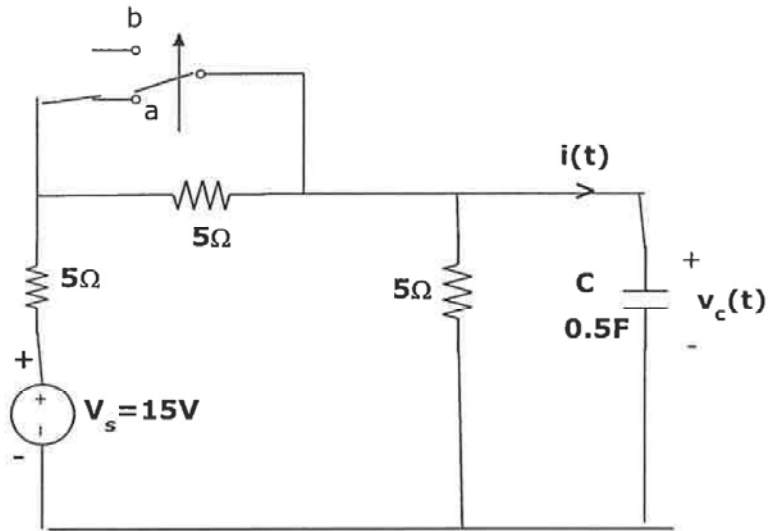


Figure-3

- Q4: (a) Thevenize (find V_{th} and Z_{th}) at terminals A –B of the circuit shown in Figure-4. [6+6]
 (c) Calculate Z_L , to be connected across the terminals A and B for maximum power dissipation in Z_L . [2]
 (b) Calculate this maximum possible power dissipation in Z_L . [6]

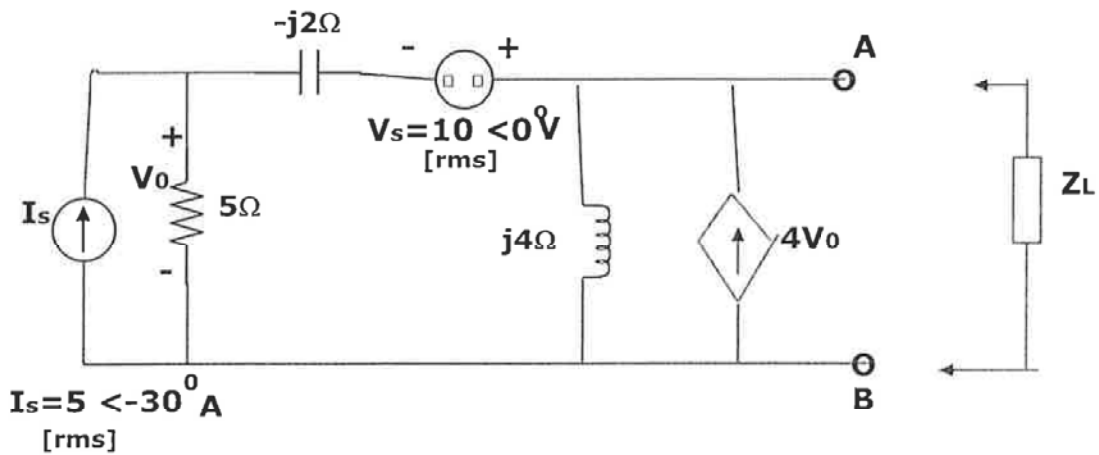


Figure-4

- Q5: (a) Write the Node Voltage equations of the following ac circuit, shown in Figure-5. [9]
- (b) Solve the node voltages $v_1(t)$, $v_2(t)$, $v_3(t)$, and find current $i_o(t)$. [9+2]

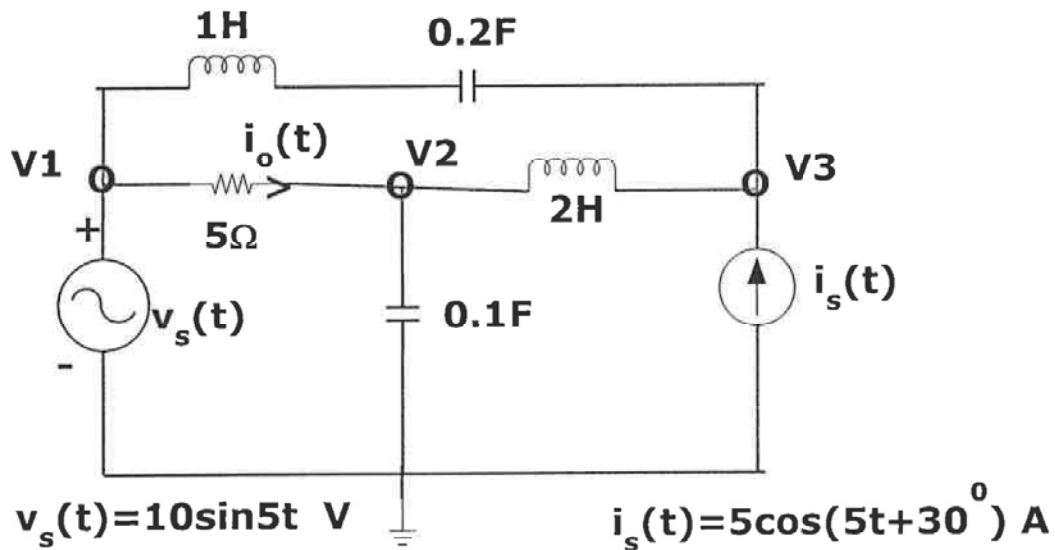


Figure-5

- Q6: (a) In the circuit shown in Figure-6, the switch was on position-a for a long time. At $t = 0$, the switch is moved to position-b. Calculate $V_c(0^+)$ and $i_L(0^+)$. [4]
- (b) Draw the Laplace Transformed circuit at $t \geq 0$. [8]
- (c) Solve $V_c(t)$. [8]

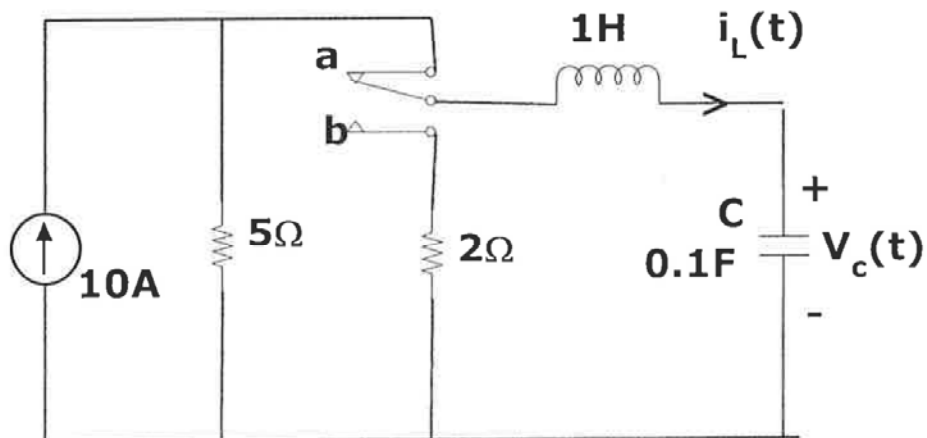
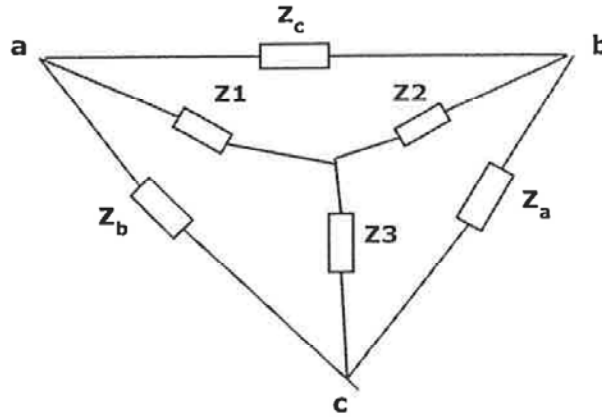


Figure-6

Appendix

Some useful Laplace Transforms:

<u>f(t)</u>	→	<u>F(s)</u>
$Ku(t)$		K/s
$\delta(t)$		1
t		$1/s^2$
$e^{-at} u(t)$		$1/(s+a)$
$\sin \omega t \cdot u(t)$		$\omega / (s^2 + \omega^2)$
$\cos \omega t \cdot u(t)$		$s / (s^2 + \omega^2)$
$e^{-\alpha t} \sin \omega t$		$\frac{\omega}{(s+\alpha)^2 + \omega^2}$
$e^{-\alpha t} \cos \omega t$		$\frac{(s+\alpha)}{(s+\alpha)^2 + \omega^2}$
$\frac{df(t)}{dt}$		$sF(s) - f(0^-)$
$\frac{d^2 f(t)}{dt^2}$		$s^2 F(s) - s f(0^-) - f'(0^-)$
$\int_{-\infty}^t f(q) dq$		$\frac{F(s)}{s} + \int_{-\infty}^0 f(q) dq$

Star – Delta conversion:

$$Z_1 = \frac{Z_b \cdot Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a \cdot Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a \cdot Z_b}{Z_a + Z_b + Z_c}$$

$$Z_a = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_3}$$