

National Examinations December 2019

**16-Elec-B8, Power Electronics and Drives**

**3 hours duration**

NOTES

1. **FIVE (5)** questions constitute a complete exam paper. All questions are of equal value.
2. Neatness is important. Start each question on a new page, and clearly indicate the question number. Only work written on the right-hand pages of the answer booklets will be marked. Use the pages on the left side for rough work only - *work presented on the left hand side pages will NOT be marked.*
3. You may use one of the approved Casio or Sharp calculators.
4. This is a closed book exam but one aid sheet (8 ½" by 11") is allowed written on both sides. **No worked-out solutions or diagrams are allowed on this sheet.**
5. All ac voltages and currents are rms values unless noted otherwise. For three-phase circuits, all voltages are line-to-line voltages unless noted otherwise, and power is total real power unless noted otherwise.
6. You are strongly encouraged to use a pencil and eraser for this exam.


**If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper a clear statement of any assumptions made.**

**Question 1**

The schematic diagram of a generator supplying two loads over a distribution system is shown below. Load A draws 8kW at a leading power factor of 0.8, while load B draws 10kW at a power factor of 0.6 lagging. The terminal voltage at load B is 215V.

Determine:

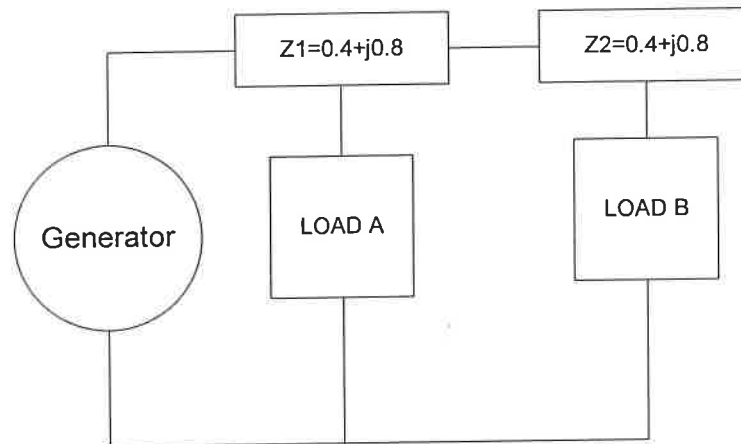- The terminal voltage at load A; and
- The apparent power, p.f. and the terminal voltage of the generator.



Schematic Diagram for Question (1)

**Question 2**

A 3 phase, 3 wire system of 208V supplies an electrical heating unit of 1500W (unity power factor) and a 5 hp induction motor with an efficiency of 87% and pf of 0.85 lagging at full load. Determine the line current if the motor is operating at rated output power of 5hp.

**Question 3**

Briefly explain the following:

- What are the different operation regions of the SCR/thyristor?
- What is latching current?
- What is holding current?
- Why is the thyristor considered a charge-controlled device?
- What are the advantages of speed control using thyristor?

**Question 4**

A single phase, 220V (rms), 60Hz source supplies a full wave ac voltage controller. The controller powers a 20hp motor whose power factor is 20 degrees. The corresponding angle 160 degrees.

- Verify that the delay angle is 40 degrees.
- Find the effective (rms) output voltage of the controller.
- Assume that the efficiency of the motor is 0.87; find the average current through each of the thyristors and the controller.

**Question 5**

The voltage to a basic chopper circuit is  $V=24V$  and the maximum allowed current is 20amps. The load consists of a series combination of  $R$  and an inductance with time constant  $\tau$ .

Complete the entries in the following table.

Case	Chopper period ( $\tau$ ) ms	On-time ( $T_{on}$ ) ms	Time constant $\tau$ (ms)	Load Resistance $R$ ( $\Omega$ )
1	2.4	1.8	1.5	?
2	?	2.4	1.45	1.25
3	1.8	?	1.5	0.9