

**NATIONAL EXAMS
MAY 2017**

98-Phys-A5: Semiconductor Devices &

Circuits Duration: 3 hours

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate must submit with the answer paper, a clear statement of any assumption(s) made.
2. Candidates may use one of two calculators, the Casio or Sharp approved models.
3. This is a **CLOSED BOOK EXAM**.
Useful constants and equations have been annexed to the exam paper.
4. **Any FIVE (5) of the SEVEN (7)** questions constitute a complete exam paper.
The first five questions as they appear in the answer book will be marked.
5. When answering questions, candidates **MUST** clearly indicate units for all parameters used or computed.

MARKING SCHEME

<i>Questions</i>	<i>Marks</i>				
1	(a) 3	(b) 3	(c) 5	(d) 5	(e) 4
2	(a) 3	(b) 6	(c) 4	(d) 7	
3	(a) 4	(b) 4	(c) 6	(d) 6	
4	(a) 3	(b) 3	(c) 5	(d) 4	(e) 5
5	(a) 8	(b) 5	(c) 2	(d) 5	
6	(a) 3	(b) 6	(c) 6	(d) 5	
7	(a) 8	(b) 8	(c) 4		

1. Figure P1 shows a silicon bar of length L and cross-sectional area of $100 \mu\text{m}^2$ connected in series with a 10V battery. The bar is doped with 10^{17} donor atoms/cm³. At 300 °K, this corresponds to an electron mobility of $700 \text{ cm}^2/\text{V}\cdot\text{s}$ and electron drift velocity saturation of 10^7 cm/s for any electrical field E exceeding $E_{\text{sat}} = 10^4 \text{ V/cm}$.

3 pts (a) Briefly explain why electron mobility would decrease if the donor concentration was augmented.

3 pts (b) Briefly explain why electron drift velocity saturates in the presence of high electrical fields.

5 pts (c) Estimate the current I in the bar when its length $L = 0.1 \text{ cm}$.

5 pts (d) Estimate the current I in the bar when its length $L = 0.5 \mu\text{m}$.

4 pts (e) Evaluate the Hall coefficient of the semiconductor bar.

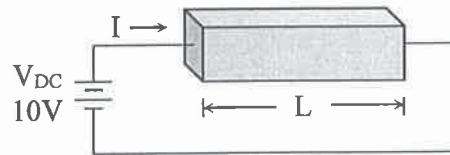


Figure P1

2. A diode is fabricated by using an abrupt silicon P-N⁺ junction formed by merging P-type and N-type semiconductors of constant cross section $A = 10^{-4} \text{ cm}^2$. The device is used in an ambient temperature of $T = 300 \text{ }^\circ\text{K}$. The equilibrium band diagram and current-voltage characteristic of the diode are shown at the right-hand side of Figure P2. The basic properties of the P-type and N-type semiconductors for a temperature of $T = 300 \text{ }^\circ\text{K}$ are shown in the table below.

P type	N type
$p_i = 2 \times 10^{10} \text{ cm}^{-3}$	$n_i = 2 \times 10^{10} \text{ cm}^{-3}$
$\tau_n = 0.1 \text{ } \mu\text{s}$	$\tau_p = 10 \text{ } \mu\text{s}$
$\mu_p = 200 \text{ cm}^2 / (\text{V}\cdot\text{s})$	$\mu_n = 1300 \text{ cm}^2 / (\text{V}\cdot\text{s})$
$\mu_n = 700 \text{ cm}^2 / (\text{V}\cdot\text{s})$	$\mu_p = 450 \text{ cm}^2 / (\text{V}\cdot\text{s})$

- 3 pts (a) Based on the band diagram, what is the value of the *contact potential* of the P-N junction?
- 6 pts (b) Evaluate the concentration of *majority* carriers, p_p and n_n , on each side of the P-N junction.
- 4 pts (c) Evaluate the concentration of *minority* carriers, n_p and p_n , on each side of the P-N junction.
- 7 pts (d) If the impurity concentrations are adjusted such that $n_p = 1.35 \times 10^5 \text{ cm}^{-3}$ and $p_n = 324 \text{ cm}^{-3}$ what is the value of the *reverse saturation current* of the P-N junction?

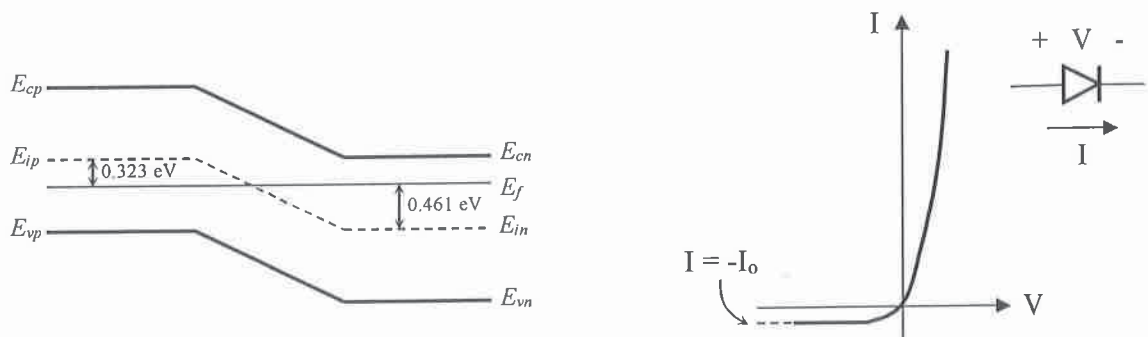


Figure P2

3. A second order high-pass *active* filter circuit is shown in Figure P3.

4 pts (a) List two advantages of *active* filters?

4 pts (b) If the OP amps are considered ideal, what are the values of input impedance R_{in} and output impedance R_{out} ?

6 pts (c) Show that the filter transfer function is given by

$$F(s) = \frac{V_3(s)}{V_1(s)} = \frac{10 s^2}{s^2 + 2\omega_o s + \omega_o^2}$$

where the *natural frequency* of the filter is given by $\omega_o = 1/RC$.

6 pts (d) Evaluate the magnitude of $F(s)$ in dB and the phase shift of $F(s)$ in degrees of this filter when the frequency of the input signal is $\omega = 0.5\omega_o$.

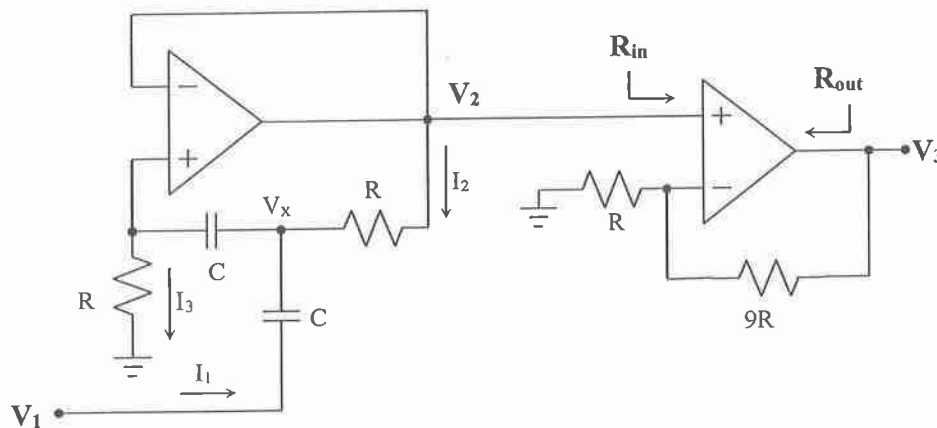


Figure P3

4. A single stage small signal amplifier is shown in Figure P4. The MOSFET device in the circuit needs to be biased such that the DC drain current $I_D = 1 \text{ mA}$ and drain-source voltage $V_{DS} = 10 \text{ V}$. To obtain these values, the gate-source voltage must be set to $V_{GS} = 1 \text{ V}$. At that operating point, the small signal parameters of the device are $g_m = 4 \text{ mA/V}$ and $r_o = 500 \text{ k}\Omega$. The low frequency response of this amplifier is given by

$$G_L(s) = A_{vm} \frac{s}{(s + \omega_{p1})} \frac{(s + \omega_z)}{(s + \omega_{p2})} \frac{s}{(s + \omega_{p3})}$$

where A_{vm} is the midband voltage gain, and

$$\omega_z = \frac{1}{R_s C_s} \quad \omega_{p1} = \frac{1}{(R_{sig} + R_{in})C_i} \quad \omega_{p2} = \frac{1}{(R_s \parallel \frac{1}{g_m})C_s} \quad \omega_{p3} = \frac{1}{(R_{out} + R_L)C_o}$$

- 3 pts (a) Briefly explain the main purpose of using capacitor C_s in the circuit of Figure P4.
- 3 pts (b) Draw the midband small signal equivalent circuit of the amplifier and show that the output resistance R_{out} of the amplifier is equal to $4.95 \text{ k}\Omega$.
- 5 pts (c) Select suitable values for resistors R_1 and R_2 to meet the following requirements:
 $V_{GS} = 1 \text{ V}$ and $R_{in} = 420 \text{ k}\Omega$
- 4 pts (d) Calculate the midband voltage gain $A_{vm} = v_o/v_{sig}$.
- 5 pts (e) If the high frequency response of this amplifier is given by $G_H(s) = A_{vm} \frac{1}{(1 + s/\omega_H)}$ where $\omega_H = 90 \text{ krad/s}$, evaluate the bandwidth of this amplifier.

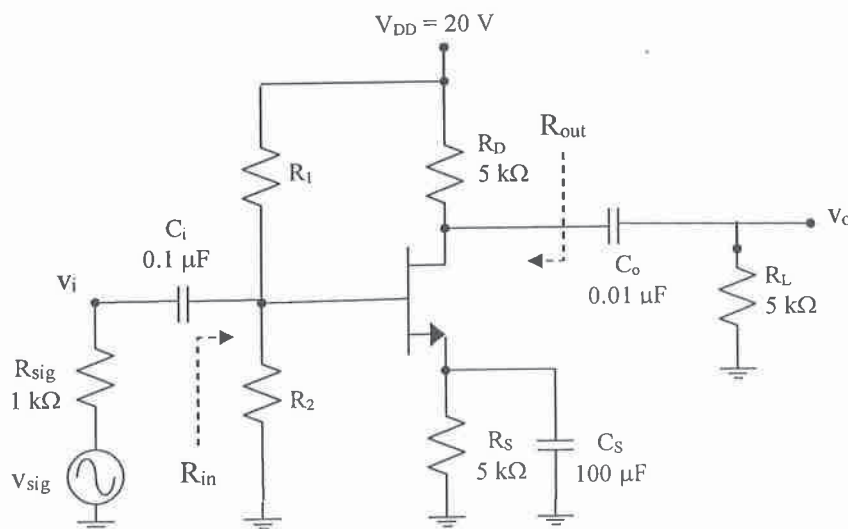


Figure P4

5. Figure P5a shows a CMOS inverter circuit and its related voltage transfer characteristic (VTC). Figure P5b shows a ring oscillator built with five identical versions of the same CMOS inverter.

- 8 pts (a) From the VTC shown in Figure P5a, graphically extract approximate values for:
- the LOW noise margin NM_L ;
 - the HIGH noise margin NM_H ;
 - the switching voltage V_x ; and
 - the small signal gain.

Briefly explain how each of the four parameters was graphically extracted.

- 5 pts (b) Calculate the exact value of the switching voltage if fabrication parametric measurements show that $k_n = 3k_p$, $V_{in} = 0.4$ V and $V_{tp} = -0.5$ V.
- 2 pts (c) Briefly explain how the inverter circuit could be modified to make the switching voltage equal to 1.5V (half the supply voltage V_{DD}).
- 5 pts (d) If the inverter is designed with timing parameters t_{phl} and t_{plh} that are equal to 1.8 ns and 2.2 ns respectively, calculate the frequency of output signal $v(t)$ coming out of node N of the ring oscillator circuit shown in Figure P5b.

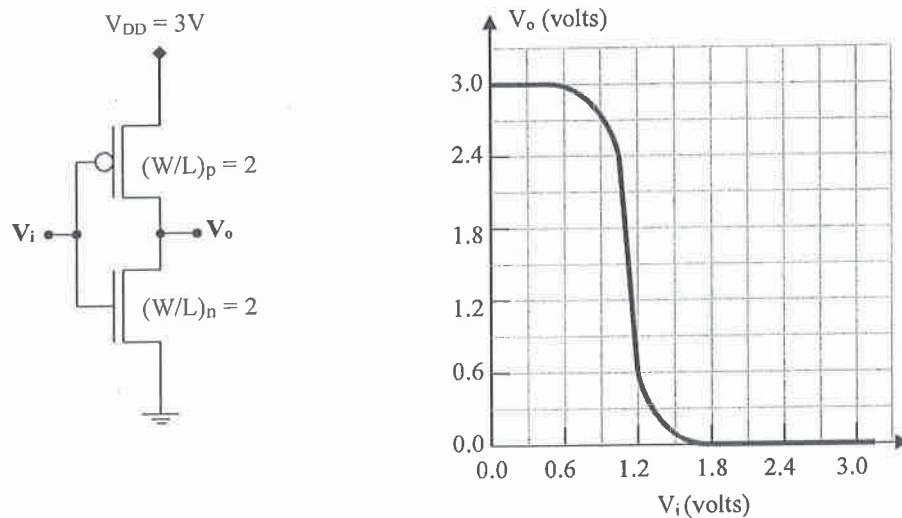


Figure P5a

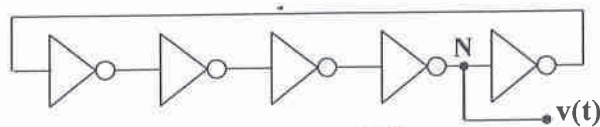


Figure P5b

6. The circuit displayed in Figure P6 receives a rapidly changing audio signal $S(t)$ and uses a three-stage n -bit analog-to-digital converter (ADC) to provide a digital signal to a processor. Maximum delays of major components of the ADC are also shown. The input signal amplitude range is $0 \leq S(t) \leq 3 \text{ V}$.

- 3 pts (a) State the name of the type of ADC circuit used and state its main disadvantage and its main advantage.
- 6 pts (b) If $V_{\text{ref}} = 3.1 \text{ V}$, determine the minimum number of bits n required to code the digital signal to obtain a resolution of at least 0.025 V .
- 6 pts (c) If the ADC is designed with $n = 8$, what would be the value of the binary (hexadecimal) code sent to the processor when the amplitude of $S(t) = 2 \text{ V}$?
- 5 pts (d) What is the maximum speed (frequency) of conversion of this ADC?

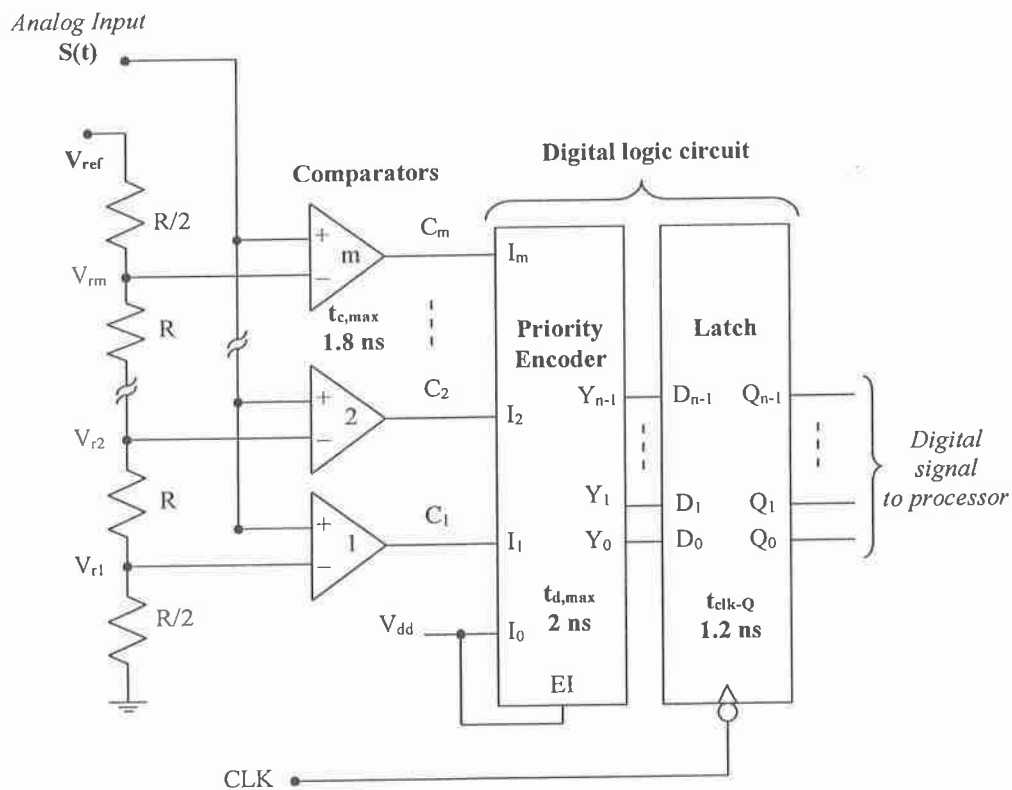


Figure P6

7. Figure P7 shows the basic diagram of a precision bridge rectifier for instrumentation applications. The OP amp is assumed to be ideal. The meter M has a coil resistance of $r = 100 \Omega$ and provides a full-scale deflection when the *average current* through it is 2 mA.

8 pts (a) Find the value of R to provide a full-scale reading when the input voltage is a sine wave of amplitude equal to 5 V.

8 pts (b) At full-scale reading, and assuming the diodes have a 0.5 V forward voltage drop, evaluate how far the maximum value of V_C is from the *saturation level* of the OP amp.

4 pts (c) If an engineer decides to use diodes with a *peak reverse voltage* (PRV) rating equal to 1 V, determine if this rating is sufficient to prevent junction breakdown at full-scale reading.

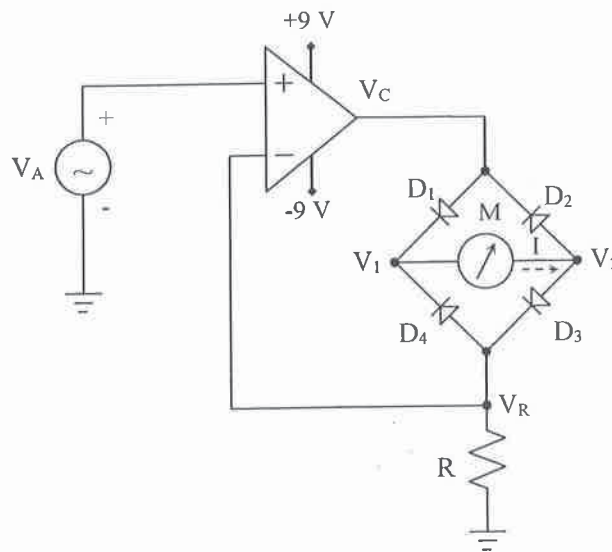


Figure P7

--- END ---

ANNEX: USEFUL CONSTANTS, EQUATIONS and MODELS

- (1) $1 \text{ \AA} = 10^{-10} \text{ m} = 10^{-8} \text{ cm} = 10^{-4} \text{ \mu m}$
 (2) $q = 1.6 \times 10^{-19} \text{ C}$
 (3) $k = 1.38 \times 10^{-23} \text{ J/}^\circ\text{K} = 8.62 \times 10^{-5} \text{ eV/}^\circ\text{K}$ [At $T = 300^\circ\text{K}$, $kT = 0.026 \text{ eV}$, $V_T = kT/q \approx 26 \text{ mV}$]
 (4) Decibel: $20 \log_{10} (V_2/V_1)$ for a voltage ratio; $10 \log_{10} (P_2/P_1)$ for a power ratio

- (5) For silicon (Si) at $T = 300^\circ\text{K}$: $n_i = 1.5 \times 10^{10}/\text{cm}^3$
 (6) $\epsilon_{\text{Si}} = 1.04 \times 10^{-12} \text{ F/cm}$
 (7) $\epsilon_{\text{SiO}_2} = 0.345 \times 10^{-12} \text{ F/cm}$ [farad: $1 \text{ F} = 1 \text{ C/V}$] [siemens: $1 \text{ mS} = 1 \text{ mA/V} = 1 \text{ mmho}$]

- (8) $f(E) = \frac{1}{1 + e^{(E-E_F)/kT}}$
 (9) $n_o + N_a = p_o + N_d$
 (10) $n_o p_o = n_i^2$
 (11) $n_o = N_c e^{(E_F - E_c)/kT} = n_i e^{(E_F - E_i)/kT}$
 (12) $p_o = N_v e^{(E_v - E_F)/kT} = n_i e^{(E_i - E_F)/kT}$
 (13) $n_i = \sqrt{N_c N_v} e^{-E_g/2kT}$
 (14) $V_o = \frac{kT}{q} \ln \frac{N_a N_d}{n_i^2}$
 (15) $W = \sqrt{\frac{2\epsilon_{\text{Si}} V_o}{q} \left(\frac{1}{N_a} + \frac{1}{N_d} \right)}$
 (16) $x_{po} = \frac{W N_d}{N_a + N_d}$ $x_{no} = \frac{W N_a}{N_a + N_d}$
 (17) $E(x) = \int \frac{\rho(x)}{\epsilon} dx$ $\phi(x) = -\int E(x) dx$

- (18) $\mu = \frac{V_{\text{drift}}}{\mathcal{E}}$
 (19) $\sigma = q(n_o \mu_n + p_o \mu_p)$

$$(20) \quad \frac{D_p}{\mu_p} = \frac{D_n}{\mu_n} = \frac{kT}{q} \quad L_n = \sqrt{D_n \tau_n} \quad L_p = \sqrt{D_p \tau_p}$$

$$(21) \quad n_n p_n = n_i^2 = n_p p_p$$

$$(22) \quad I = I_o (e^{\frac{qV}{kT}} - 1) = qA \left(\frac{D_p}{L_p} p_n + \frac{D_n}{L_n} n_p \right) (e^{\frac{qV}{kT}} - 1)$$

$$(23) \quad J = \frac{I}{A} = \sigma \mathcal{E}$$

$$(24) \quad R = \frac{L}{\sigma A}$$

$$(25) \quad R_H = \frac{1}{q(p_o - n_o)}$$


BJT relationships and model

$$(26) \quad I_C = \beta I_B \quad \text{where } \beta = I_C / I_B$$


$$(27) \quad I_E = I_B + I_C$$

$$(28) \quad g_m = I_C / V_T$$

$$(29) \quad r_\pi = V_T / I_B$$

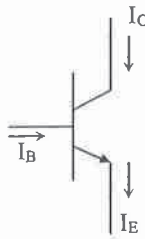

Small signal BJT model

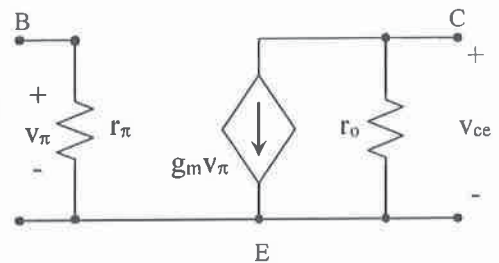

MOS device in a p substrate

$$(30) \quad \phi_F = \frac{kT}{q} \ln \frac{N_a}{n_i}$$

$$(31) \quad W_m = 2 \sqrt{\frac{\epsilon_{Si} \phi_F}{q N_a}}$$

$$(32) \quad Q_d = -q N_a W_m$$

$$(33) \quad C_i = \frac{\epsilon_{SiO_2}}{d}$$

$$(34) \quad V_T = \Phi_{ms} + 2\phi_F - \frac{1}{C_i} (Q_i + Q_d)$$

MOSFET symbols, relationships and model

(35) $g_m = \frac{\partial I_D}{\partial V_{GS}}$

(36) $k_n = \mu_n C_{ox}(W/L)_n$



(37) $k_p = \mu_p C_{ox}(W/L)_p$

(38) $I_{Dn} = (k_n/2) (V_{GSn} - V_{tn})^2$ when $V_{DSn} > V_{GSn} - V_{tn}$


(39) $I_{Dn} = (k_n/2) [2(V_{GSn} - V_{tn})(V_{DSn}) - (V_{DSn})^2]$ when $V_{DSn} < V_{GSn} - V_{tn}$

(40) $I_{Dp} = (k_p/2) (V_{GSp} - V_{tp})^2$ when $V_{DSp} < V_{GSp} - V_{tp}$

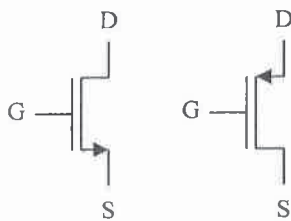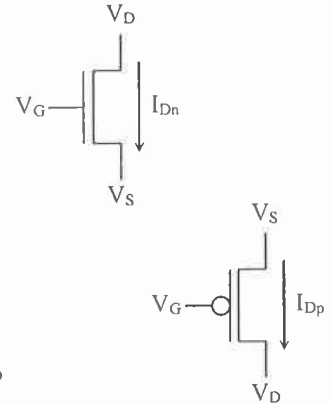(41) $I_{Dp} = (k_p/2) [2(V_{GSp} - V_{tp})(V_{DSp}) - (V_{DSp})^2]$ when $V_{DSp} > V_{GSp} - V_{tp}$



*MOSFET
small signal
model*

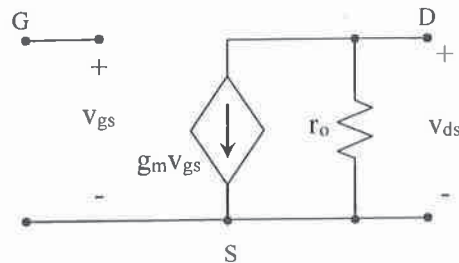

(42) For a complex number $R = A + Bj$, $|R| = (A^2+B^2)^{1/2}$ and $\phi(R) = \tan^{-1}(B/A)$

(43) $V_o(t) = -\frac{1}{RC} \int_0^T V_i(t) dt$ $\frac{V_o(s)}{V_i(s)} = \frac{-1}{sRC}$ [integrator circuit]

(44) $V_{DC} \equiv V_{average} = \frac{1}{T} \int_0^T V(t) dt$ = V_p/π for a half-wave sinewave and $2V_p/\pi$ for full-wave sinewave

(45) $V_{rms} = \sqrt{\frac{1}{T} \int_0^T [V(t)]^2 dt}$ = $\frac{V_p}{2}$ for a half-wave sinewave and $\frac{V_p}{\sqrt{2}}$ for full-wave sinewave